

# **Analog and Digital Electronics Lab (EC13203)**

**IT-B1**

**Lab-4**

**(Design of Half Subtractor and Full  
Subtractor by using Basic  
Gates/Universal Gate)**


Dr. Anand Sharma

Assistant Professor

ECED, MNNIT Allahabad

# Half Subtractor


Block Diagram

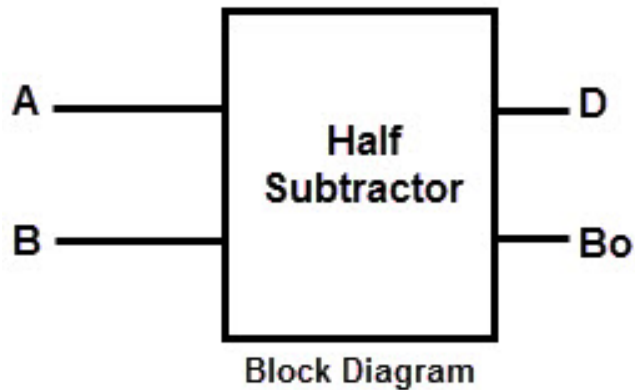

Truth Table


A	B	D	B <sub>0</sub>
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Implementation with basic logic gates

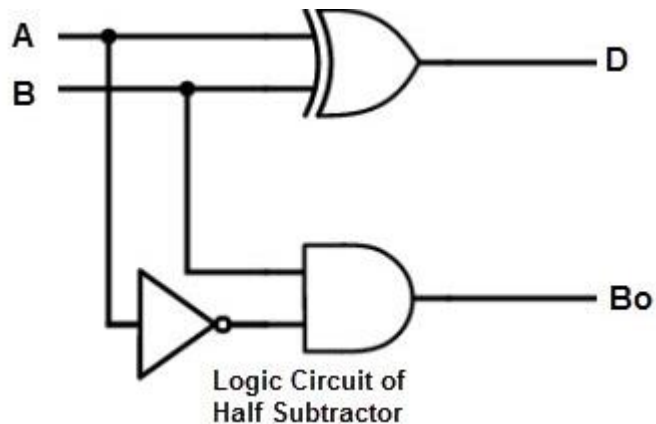


# Cont....
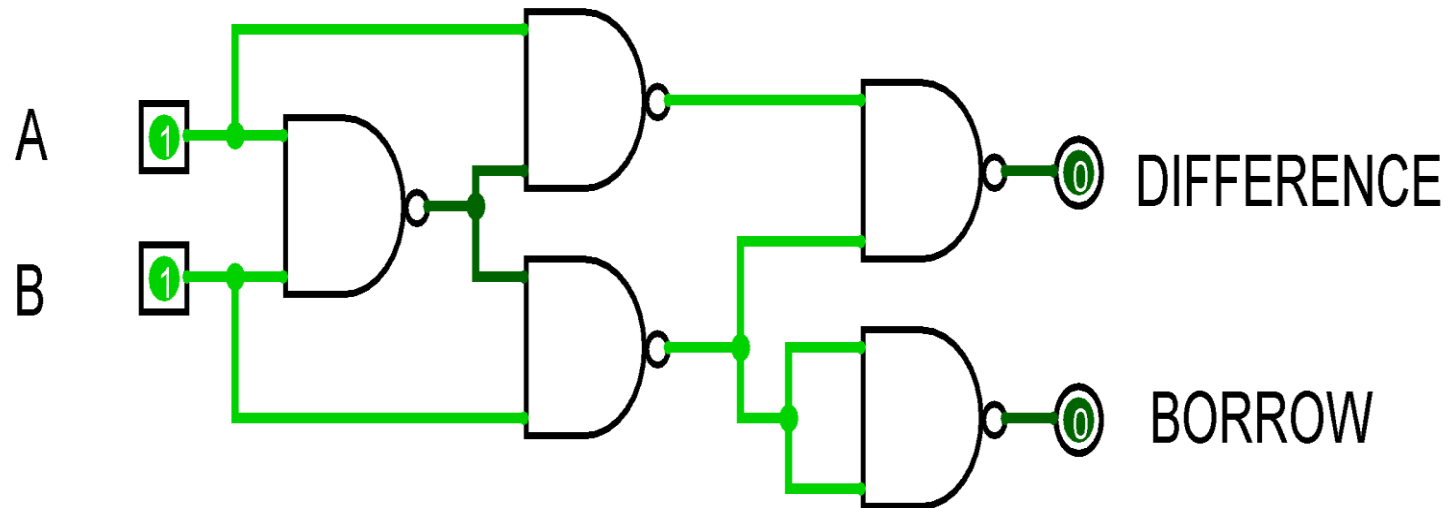
## Implementation with Universal logic gates



# Full Subtractor


## Block Diagram

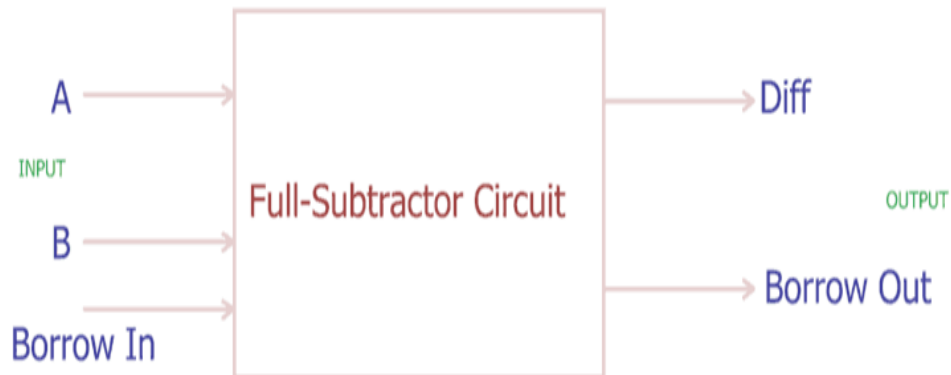

## Truth Table


A	B	C	D	BO
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

## Implementation with basic logic gates

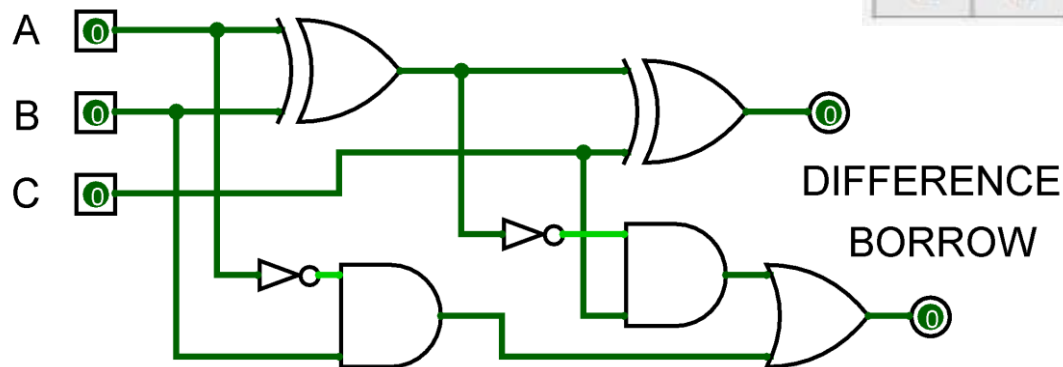


Cont....
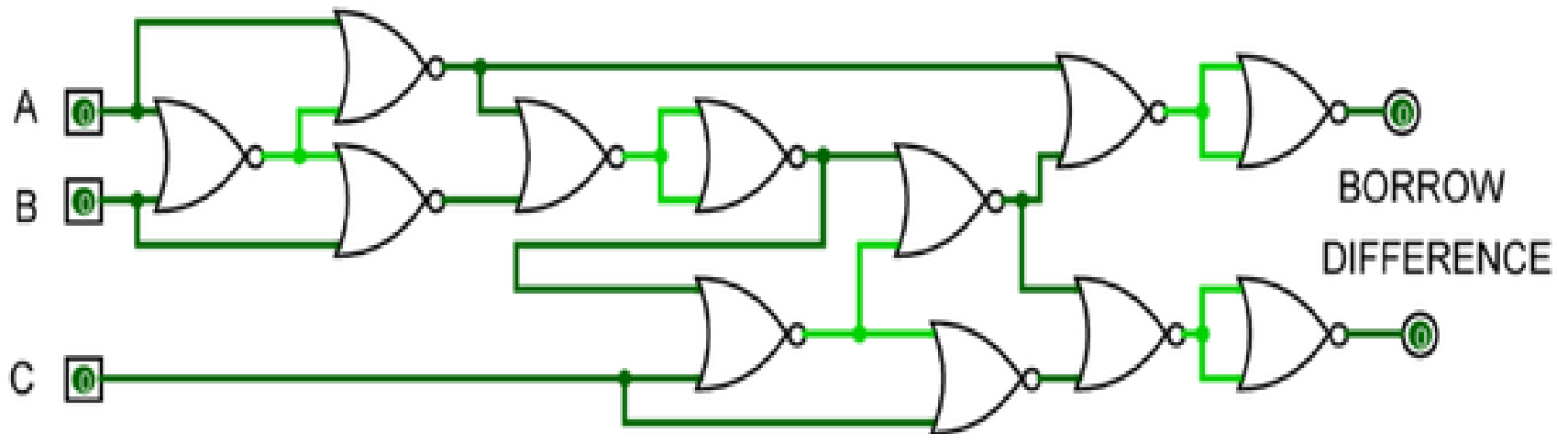
## Implementation with Universal logic gates



# 4-bit Adder

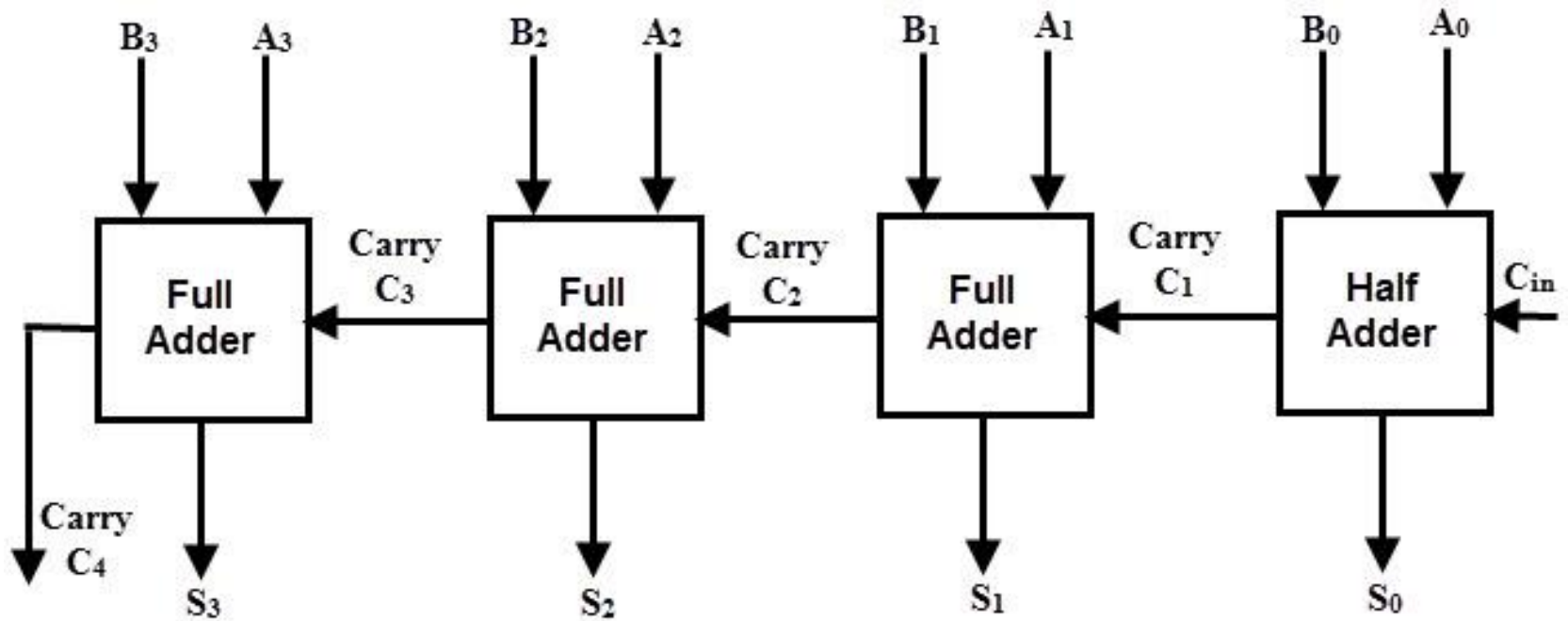

# Gate Level Diagram of 4-bit Adder

