

Date: 11/08/2020

## Experiment No. 1

**Aim:** To design and verify Full Adder using basic gates.

**Tool & Apparatus Used:** LTspice, ICs Number

**Theory:** The Full Adder is an arithmetic circuits....

**Fig.1.1** Circuit diagram of Full Adder

**Table 1.1** Truth Table of Full Adder


**Design and Simulation:**

**Figure 1.2** Schematic of Full Adder

**Observation:**

**Figure 1.3** Transient result of Full Adder output

**Result:** The Full Adder has been designed using basic gates and output and truth table are verified.

**Applications:** In ALUs, Computers, Microprocessors

## Table of Contains

[illegible]