

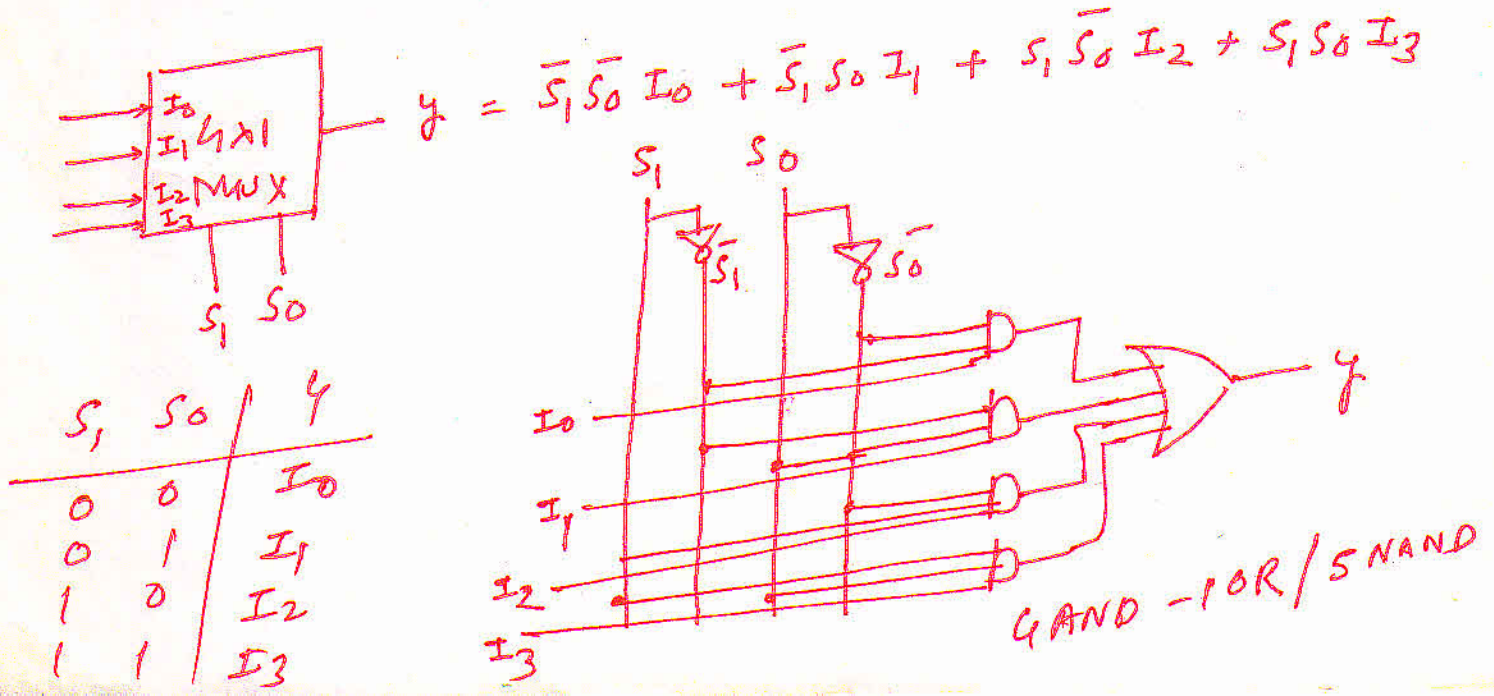

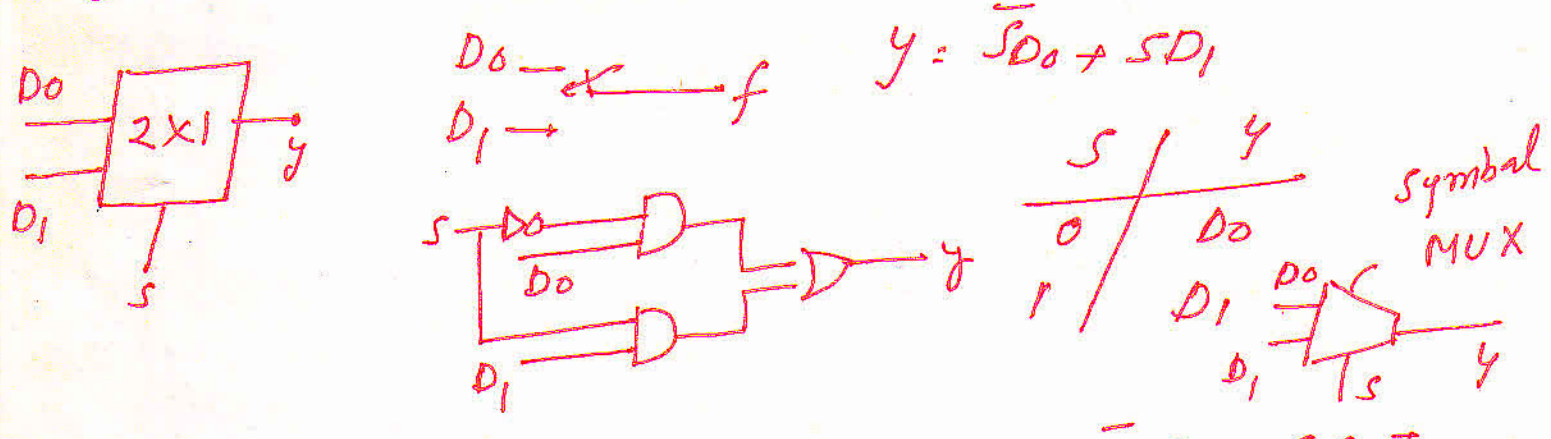
# Multiplexer / Data Selector  $\rightarrow$  It is a Combinational Circuit that Selects binary Information from one of multiple input lines and connects it to a single output line. The Connection of a particular input line to output line is controlled by a set of Select / Control lines.

- \* for  $2^n$  input lines,  $n$  select / control lines are required.
- \* This is in fact one way rotary switch.
- \* It does (PISO) Parallel in Serial out data operation.
- \* Additionally Mux has a strobe / enable input for ease in cascading mux.


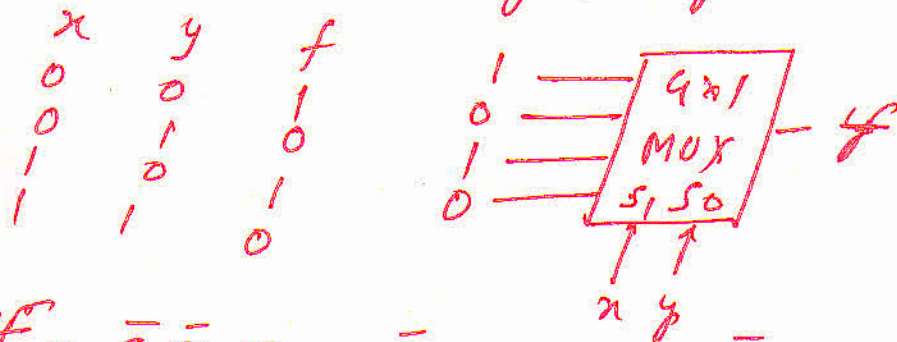
# Implement  $f(x, y) = \Sigma(0, 2)$   
 $= \bar{x}\bar{y} + x\bar{y}$



$$S_1 = x, S_0 = y$$

$$f = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$

$$= \bar{x}\bar{y}(1) + \bar{x}y(0) + x\bar{y}(1) + xy(0)$$

$$= \bar{x}\bar{y} + x\bar{y}$$

\* However a Boolean function involving 3 Variable may also be implemented using 4x1 MUX


e.g.  $f(x, y, z) = \bar{x}\bar{y}z + \bar{x}yz + x\bar{y}z + xyz$   
 $= \Sigma(1, 3, 5, 7)$

Comparing  $y_{MUX} = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$

take  $y = S_1, z = S_0$

$$y_{MUX} = \bar{y}\bar{z}I_0 + \bar{y}zI_1 + y\bar{z}I_2 + yzI_3$$

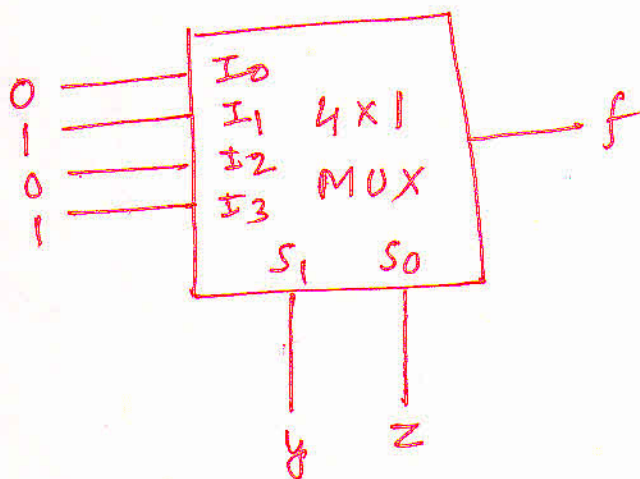$I_0 = 0, I_1 = (x + \bar{x}) = 1, I_2 = 0, I_3 = x + \bar{x} = 1$






⇒ Alternatively → out of  $n$  variable connect  $(n-1)$  variables to select lines.

$$f(x, y, z) = \Sigma(1, 3, 5, 7)$$


Consider  $y$  and  $z$  select lines.  $y = S_1, z = S_0$

	$\bar{y}\bar{z}$ $I_0$	$\bar{y}z$ $I_1$	$y\bar{z}$ $I_2$	$yz$ $I_3$	
$\bar{x}$	0	①	2	③	both are encode → 1
$x$	4	⑤	6	⑦	Non " " → 0
	0	1	0	1	Top is encode = $\bar{x}$
					bottom " " = $x$

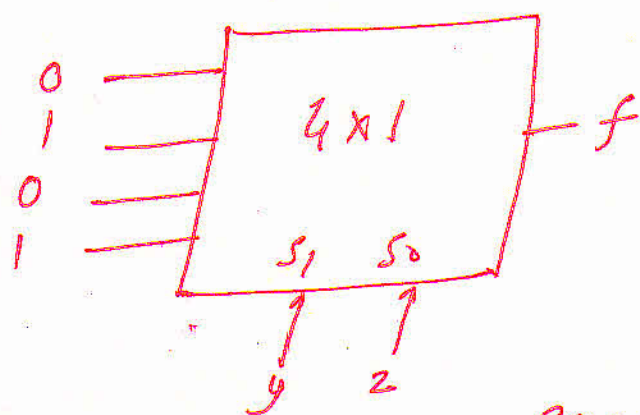


\* The Variable that are connected to select lines are arbitrary.  $x = S_1, y = S_0$

	$\bar{x}\bar{y}$ $I_0$	$\bar{x}y$ $I_1$	$x\bar{y}$ $I_2$	$xy$ $I_3$
$\bar{z}$	0	2	4	6
$z$	①	③	⑤	⑦
	$\bar{z}$	$z$	$\bar{z}$	$z$

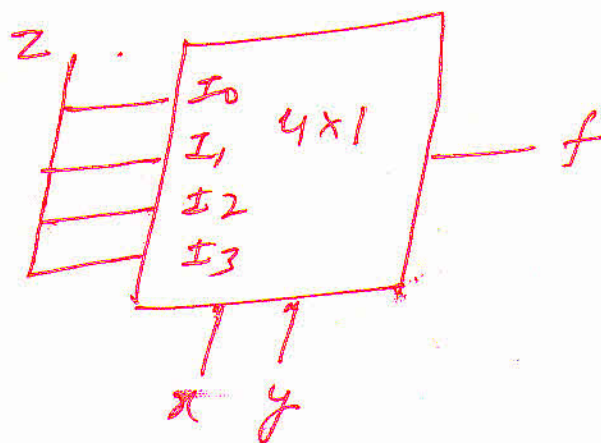

\* If  $x = S_1, z = S_0$

	$\bar{x}\bar{z}$ $I_0$	$\bar{x}z$ $I_1$	$x\bar{z}$ $I_2$	$xz$ $I_3$
$\bar{y}$	0	①	4	⑤
$y$	2	③	6	⑦
	0	1	0	1

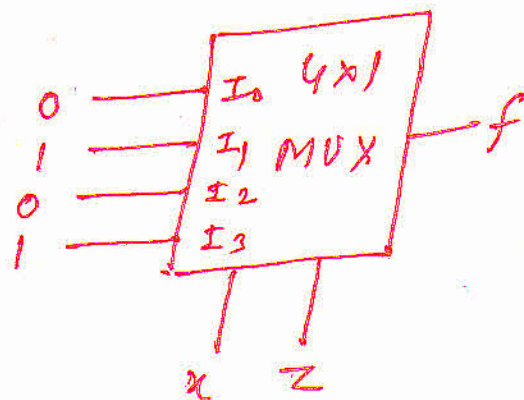


⇒ Implement function

$$f = \Sigma(0, 2, 3, 5, 7) \text{ using } 8 \times 1 \text{ MUX}$$

Since the function involve 3 variables i.e.  $f(a, b, c)$


Implementation is straight forward

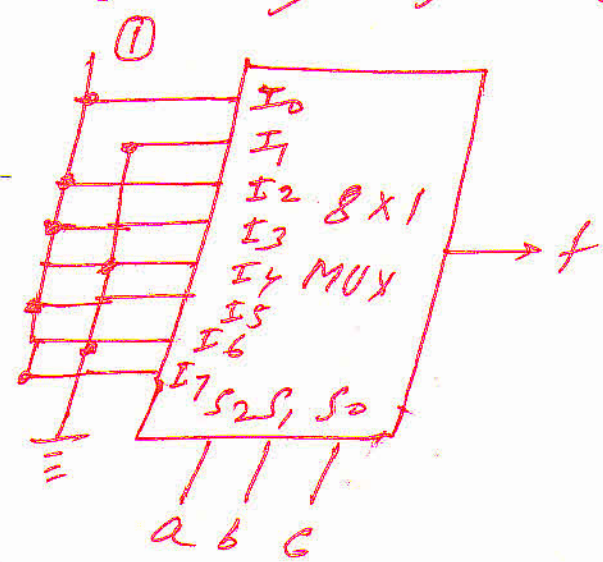

• Implement  $f(a, b, c, d) = \Sigma(2, 4, 5, 7, 10, 14)$

$$S_2 = a, S_1 = b, S_0 = c$$

	$\bar{a}\bar{b}\bar{c}$ $I_0$	$\bar{a}\bar{b}c$ $I_1$	$\bar{a}b\bar{c}$ $I_2$	$\bar{a}bc$ $I_3$	$a\bar{b}\bar{c}$ $I_4$	$a\bar{b}c$ $I_5$	$ab\bar{c}$ $I_6$	$abc$ $I_7$
$\bar{d}$	0	②	④	6	8	⑩	12	⑭
$d$	1	3	⑤	⑦	9	11	13	15
	0	$\bar{d}$	1	$d$	0	$\bar{d}$	0	$\bar{d}$

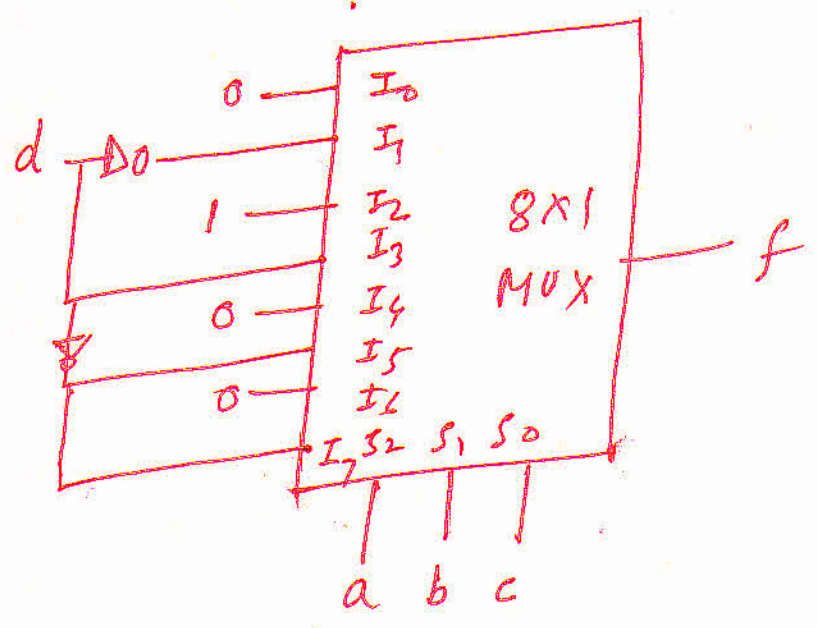




\* Implement a Sequence generator to generate a sequence of unique 16 bits

1011001110111011

⇒ It is required to Cascade two 8x1 MUX


\* UPPER MUX is enabled if  $A = 0$

\* Lower MUX is enabled if  $A = 1$

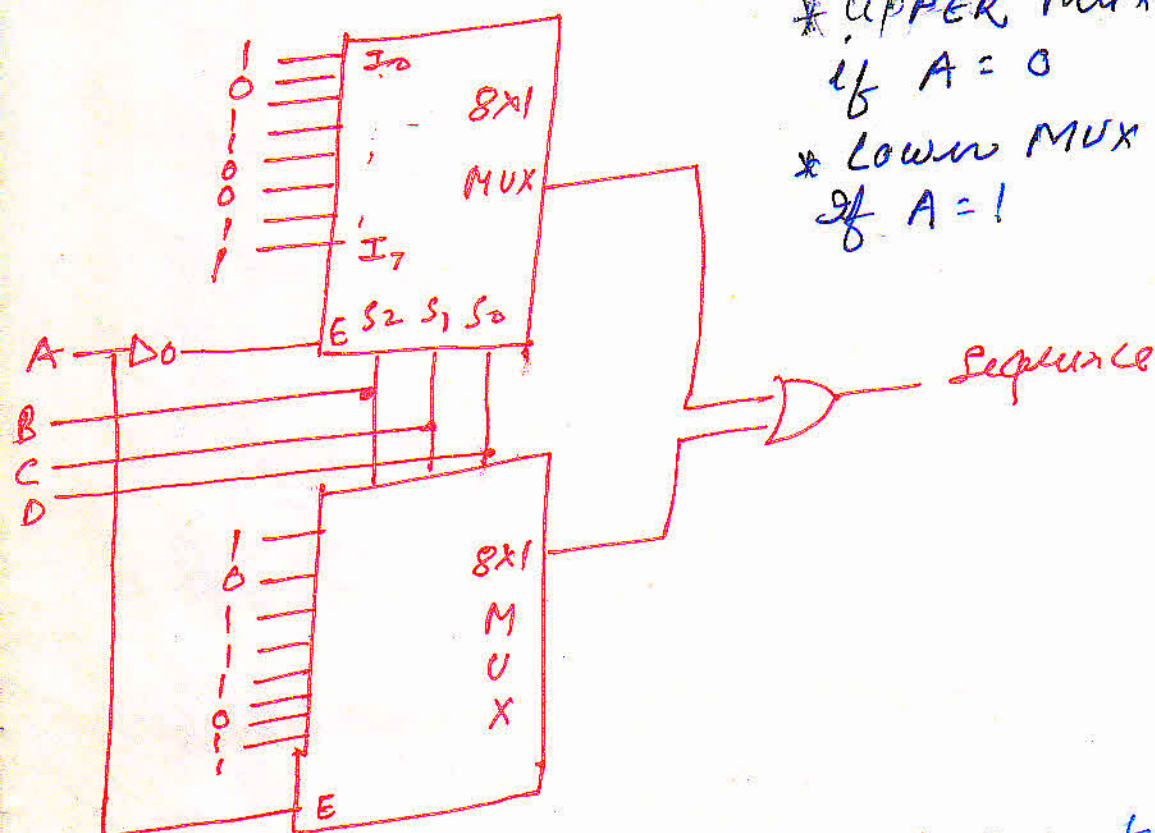
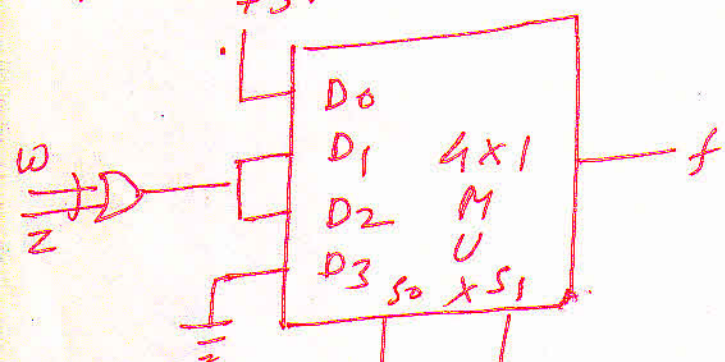
# find the function Realized by given fig in Min terms.

$$f = \bar{x}\bar{y}D_0 + \bar{x}yD_1 + x\bar{y}D_2 + xyD_3$$



$$= \bar{x}\bar{y}(1) + \bar{x}y(\omega \oplus z) + x\bar{y}(\omega \oplus z) + xy(0)$$


$$= \bar{x}\bar{y} + \bar{x}y[\omega\bar{z} + \bar{\omega}z] + x\bar{y}[\omega\bar{z} + \bar{\omega}z] + 0$$

$$= \bar{x}\bar{y} + \bar{x}y\omega\bar{z} + \bar{\omega}\bar{x}yz + \omega x\bar{y}\bar{z} + \bar{\omega}x\bar{y}z$$

$$f = \sum_{\substack{2 \\ 6}} (0, 1, 3, 5, 8, 9, 10, 12)$$


	$\bar{y}z$	$\bar{y}\bar{z}$	$yz$	$y\bar{z}$
$\bar{\omega}\bar{x}$	1	1	1	
$\bar{\omega}x$		1		
$\omega\bar{x}$	1			
$\omega x$	1	1		1
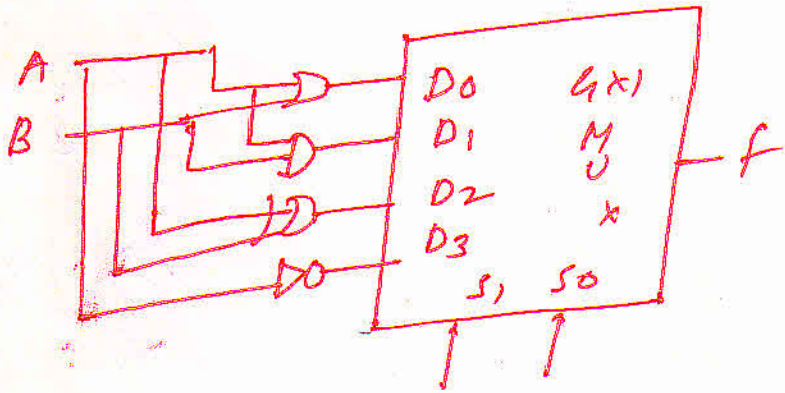
# Use 4x1 to perform 4 operation.  $A \cdot B$   
 $A+B$   $A \oplus B$   $\bar{A}$



$S_1$	$S_0$	operation
0	0	$A+B$
0	1	$A \cdot B$
1	0	$A \oplus B$
1	1	$\bar{A}$

# find function  $f(x, y)$

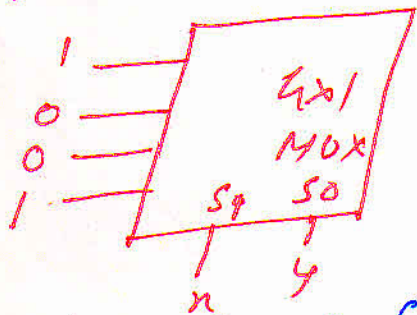


$$f = \bar{x}\bar{y}(1) + \bar{x}y(0) + x\bar{y}(0) + xy(1)$$

$$f = \bar{x}\bar{y} + x\bar{y} = \bar{x} \oplus \bar{y} = x \odot y$$


# Find function  $f$

$$\bar{a} \cdot 0 + a \cdot 1 = a$$

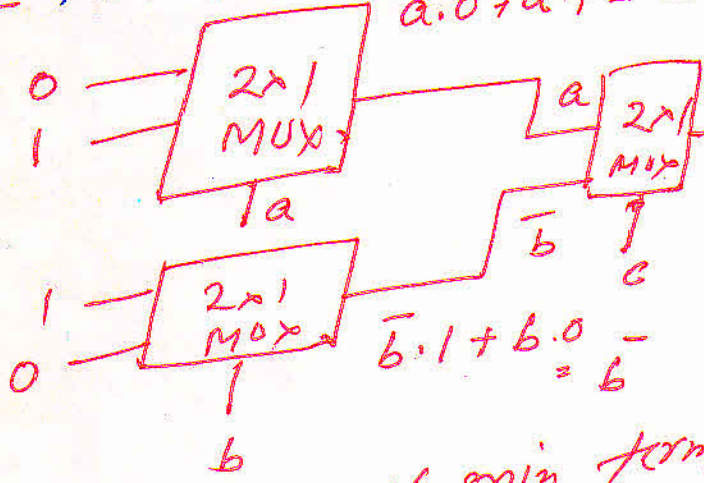

$$f = \bar{c}a + c\bar{b}$$
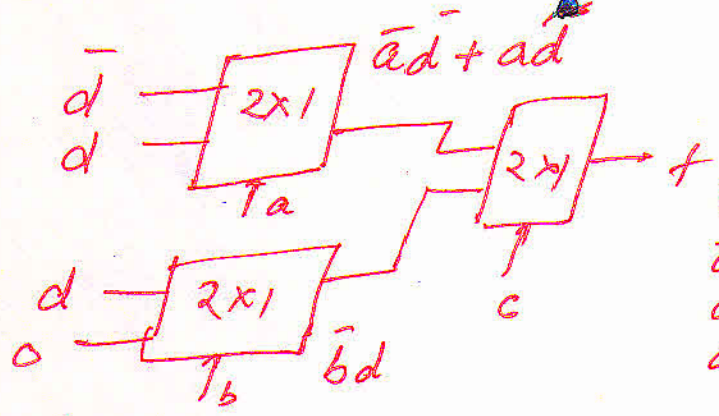
# find the No. of min term in the given function.



$$(\bar{a}d + ad)\bar{c} + \bar{b}dc = f$$


$$\bar{a}\bar{c}d + a\bar{c}d + \bar{b}cd = f$$

$\bar{a}\bar{b}$	1		1	
$\bar{a}b$	1			
$ab$		1	1	
$a\bar{b}$		1	1	
	$\bar{c}\bar{d}$	$\bar{c}d$	$cd$	$c\bar{d}$


$$f = \Sigma(0, 3, 4, 9, 11, 13) = \underline{6 \text{ min terms}}$$



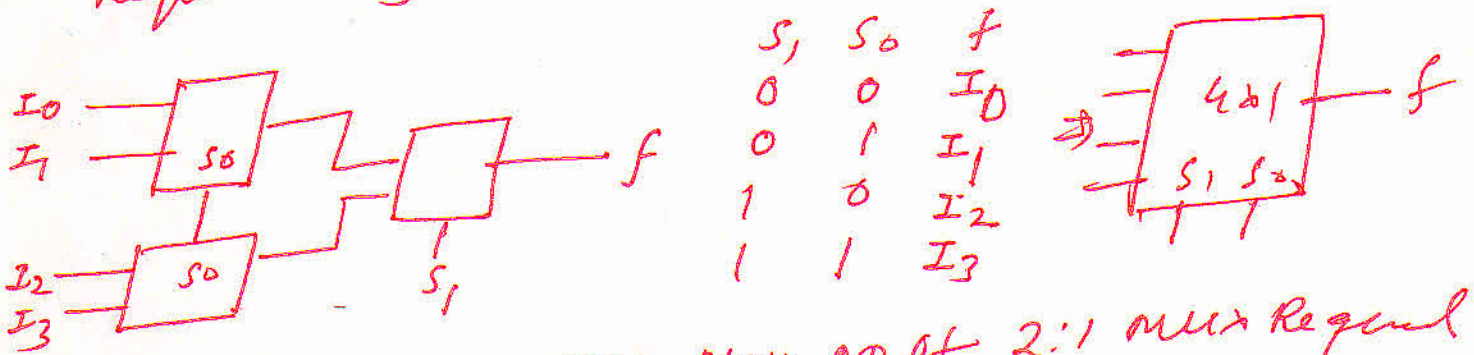
# To Implement  $4 \times 1$  MUX MIN. NO. of  $2:1$  MUX  
 Required : 3


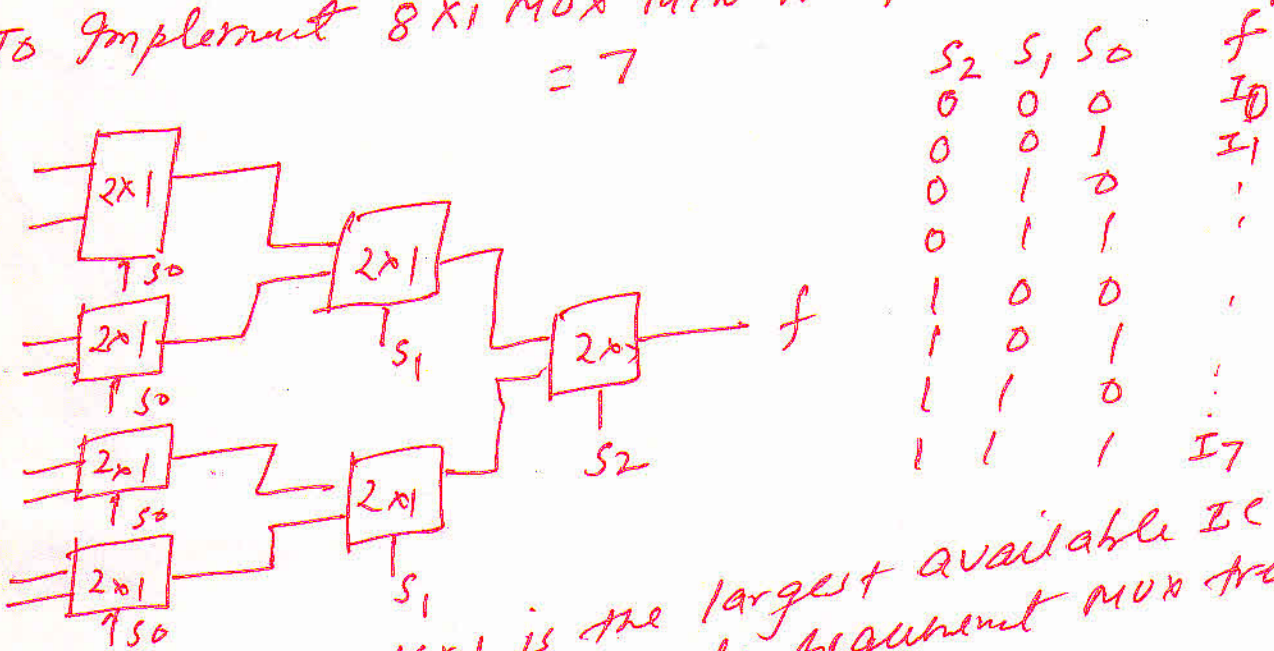
# To Implement  $8 \times 1$  MUX MIN NO of  $2:1$  MUX Required  
 = 7



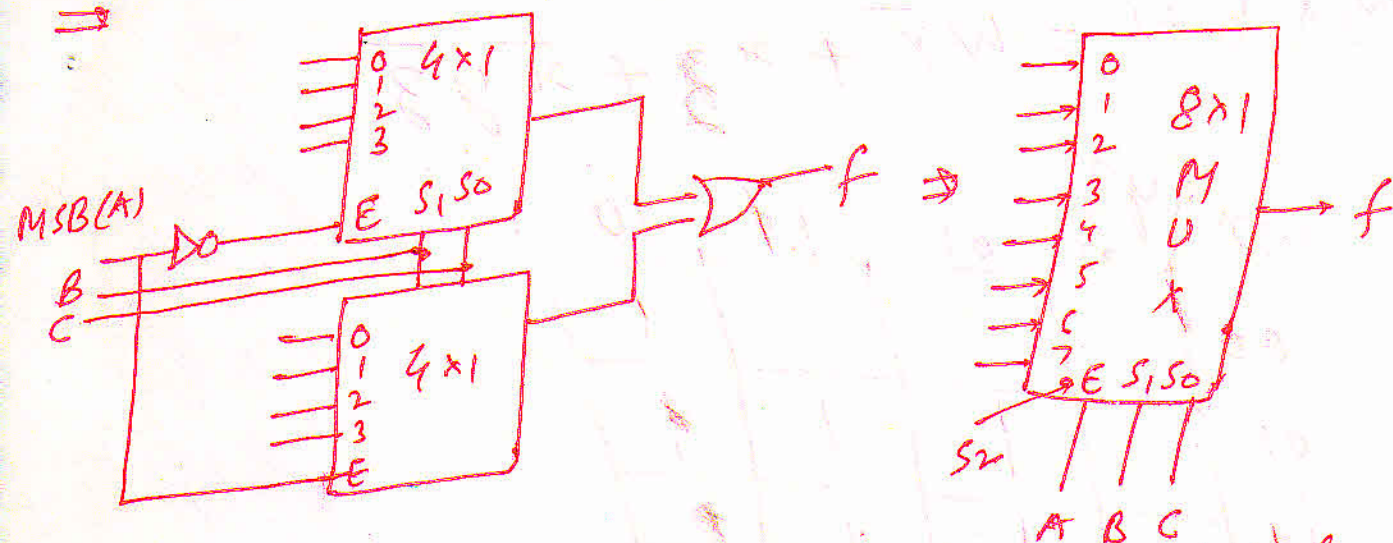
# MUX Tree  $\rightarrow 16 \times 1$  is the largest available i.e. To meet large no. of input requirement MUX tree is formed  
 MUX has an enable (also called strobe) input to control unit operation. The enable input may also be used to expand no. of inputs (Cascading)  
 The cascading taken care of the fact that MSB is always 0 for first half of the min terms. and 1 for remaining half. The MSB is therefore connected to enable input of the MUX  
 $\Rightarrow 4 \times 1$  may be cascaded to form  $8 \times 1$  MUX.




⇒ Similarly two 8x1 MUX may be cascaded to form 16x1 MUX.


⇒ 8x1 using 4x1

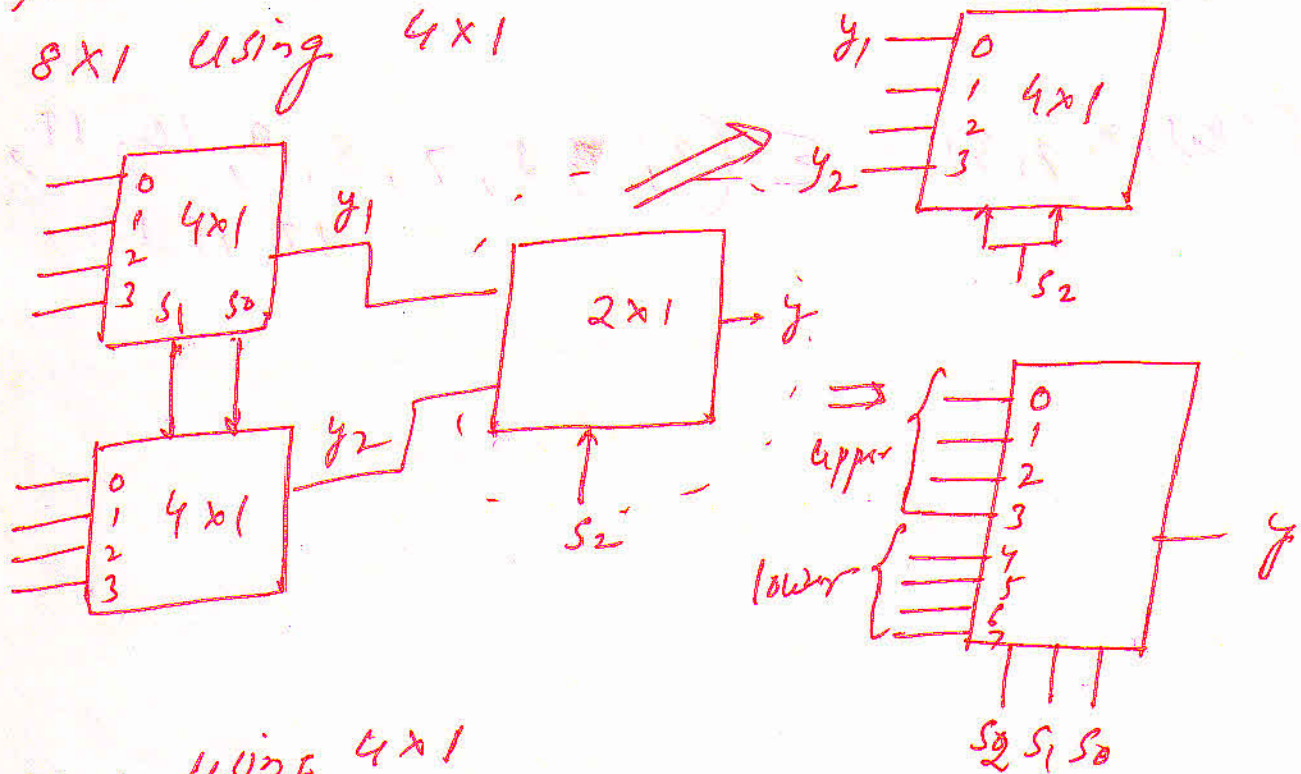

⇒ 16x1 using 4x1

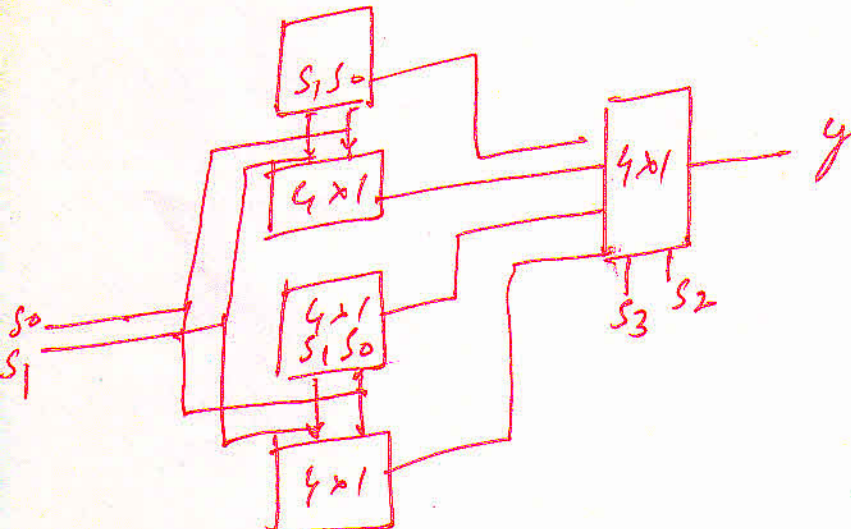

⇒ 16x1 using 8x1 and 2x1

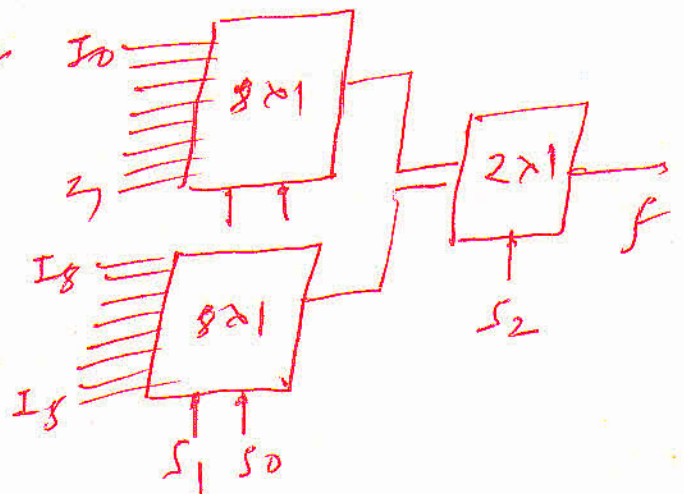



⇒ 16x1 MUX using 2x1

$$8 + 4 + 2 + 1 = 15 \text{ MUX } (2 \times 1)$$

$\begin{matrix} 1 & 1 & 1 & 1 \\ s_0 & s_1 & s_2 & s_3 \end{matrix}$

⇒ To implement using.

4:1 MUX	$\xrightarrow{3}$	2:1
8:1 "	$\xrightarrow{7}$	2:1
16:1 "	$\xrightarrow{15}$	2:1
256:1	$\xrightarrow{255}$	2:1
$2^n:1$	$\xrightarrow{2^n-1}$	2:1

$$\frac{256}{2} \quad \frac{128}{2} \quad \frac{64}{2} \quad \frac{32}{2} \quad \frac{16}{2} \quad \frac{8}{2} \quad \frac{4}{2} \quad \frac{2}{2}$$

$$128 + 64 + 32 + 16 + 8 + 4 + 2 + 1 \quad \begin{matrix} \text{4:1} = 3 \\ \text{8:1} = 7 \end{matrix}$$

⇒ To implement using

8:1	$\xrightarrow{3}$	4:1	1024:1 $\rightarrow$ 4:1
16:1	$\xrightarrow{5}$	4:1	
64:1	$\xrightarrow{21}$	4:1	
256:1	$\xrightarrow{85}$	4:1	

$$\frac{256}{4} \quad \frac{128}{4} \quad \frac{64}{4} \quad \frac{32}{4} \quad \frac{16}{4} \quad \frac{8}{4} \quad \frac{4}{4} \quad \frac{2}{4}$$


$$64 + 32 + 16 + 8 + 4 + 2 + 1 \quad \begin{matrix} \text{8:1} = 3 \\ \text{16:1} = 7 \end{matrix}$$

⇒ 256x1 using 8x1 = 32 + 4 = 36 (8x1) and 1. 4x1 MUX = 37


# Note:





(i) MUX is also known as Universal logic circuit

(ii) 2x1 MUX is " " " " BUFFER

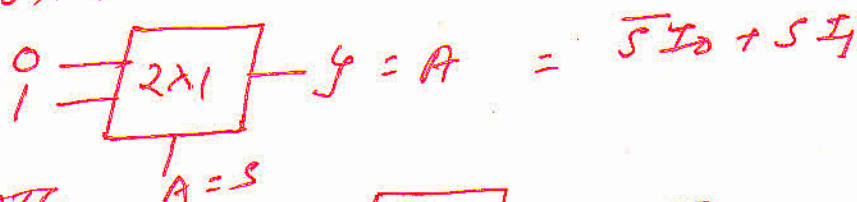


(iii) NOT GATE

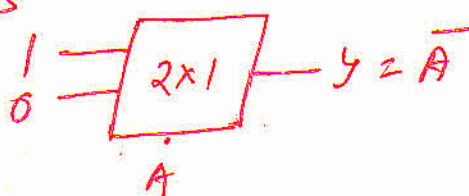

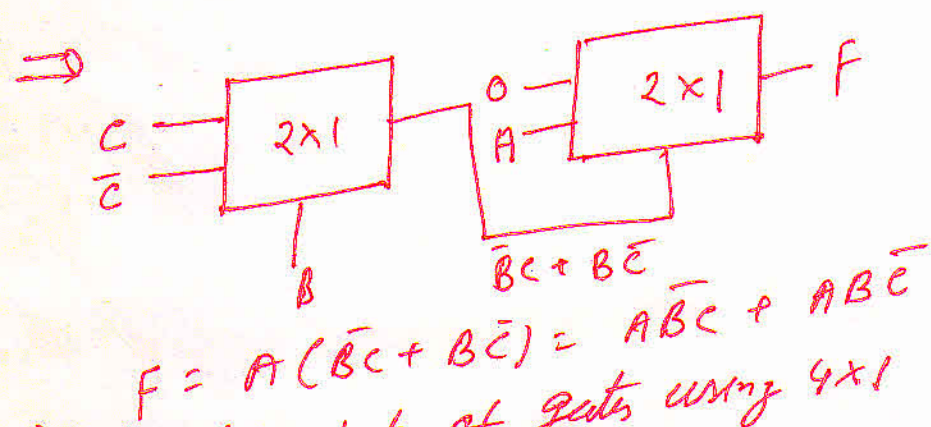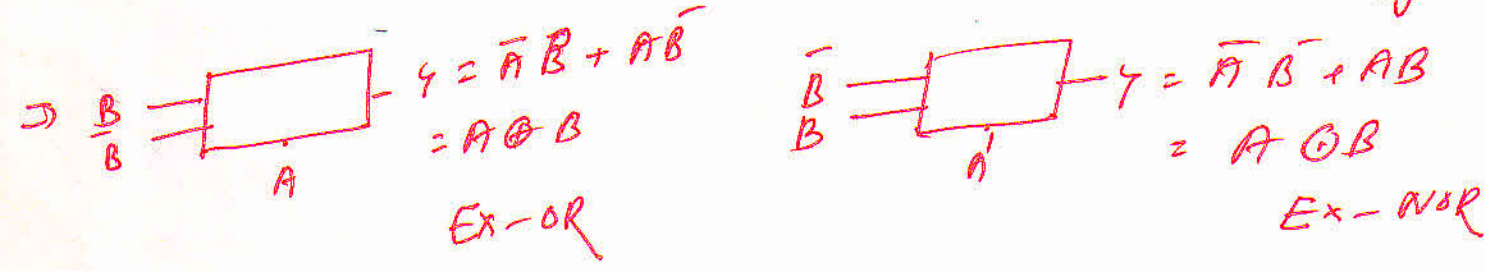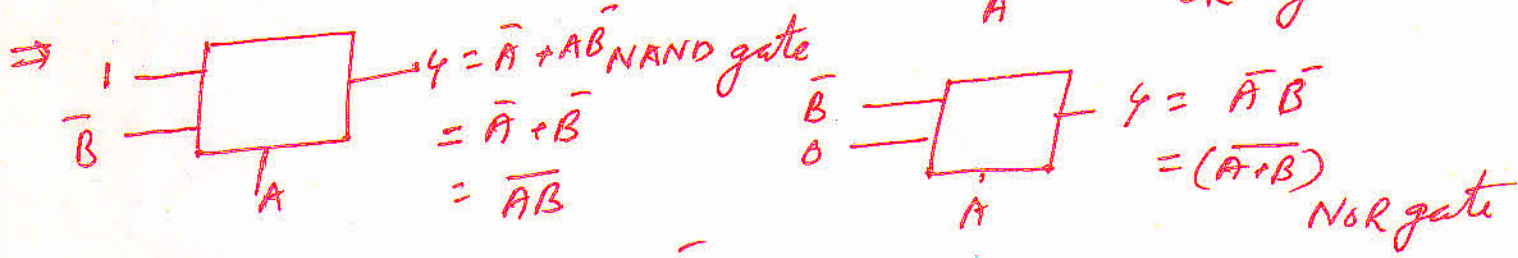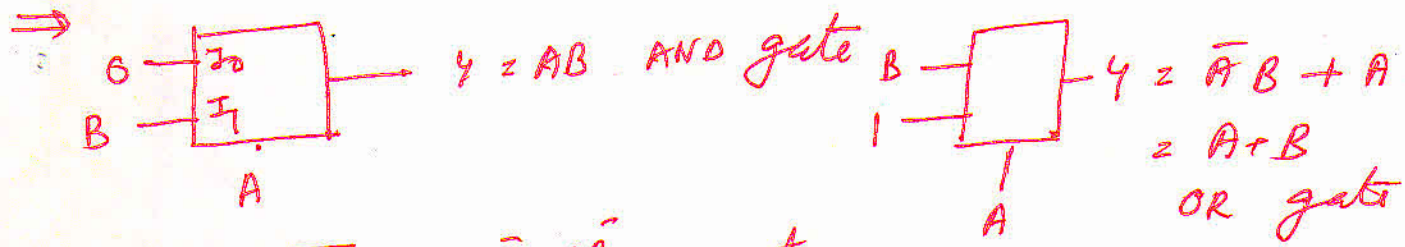

⇒ Implementation of gates using 4x1

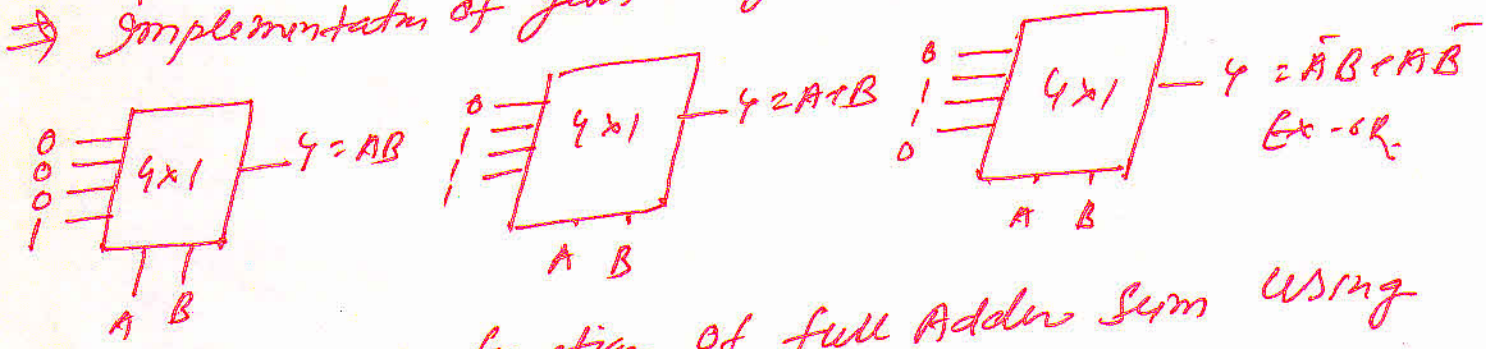

# Implement a function of full Adder Sum using 4x1 MUX.

$f = \Sigma(1, 2, 4, 7)$

	$I_0$	$I_1$	$I_2$	$I_3$
$\bar{C}$	0	②	④	6
$C$	①	3	5	⑦
	$C$	$\bar{C}$	$\bar{C}$	$C$

$f$