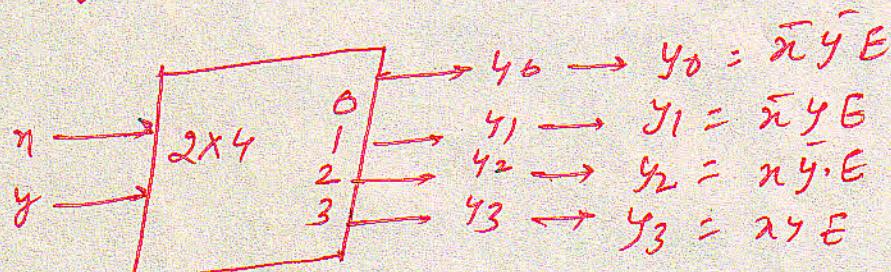



Decoder → Decoder is a combination ext that convert binary information from n input lines to a maximum of 2^n unique output lines. In general decoder is n to m line converter $m \leq 2^n$ (If some unused or don't care conditions. Most. If not all decoder also include one or more enable input to control the ext operation and assist cascading.

⇒ 2×4 decoder with active high o/p




E (active high enable),


E	x	y	y ₀	y ₁	y ₂	y ₃
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
	0	x	x	0	0	0

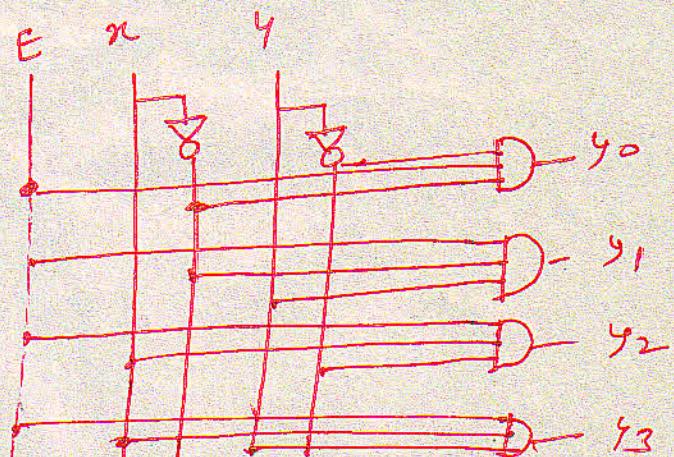

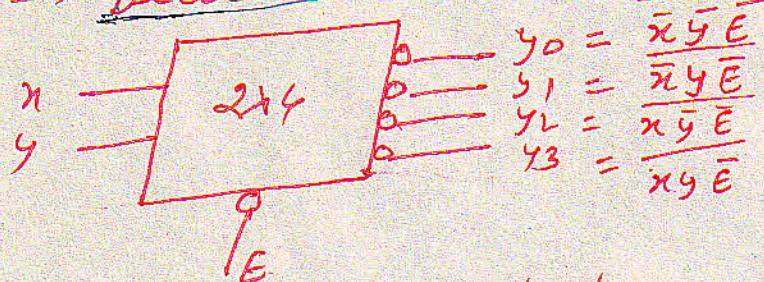⇒ Decoder with active low o/p and active low enable




E	x	y	y ₀	y ₁	y ₂	y ₃
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	x	x	1	1	1	1

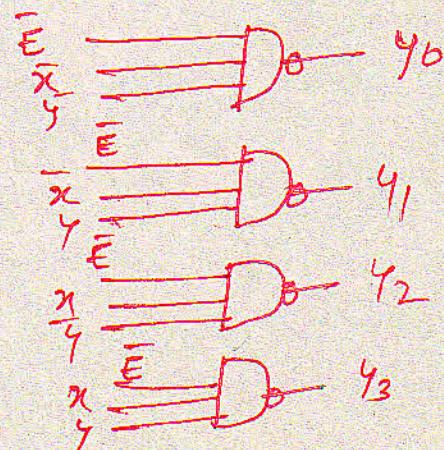

Demultiplexer (SIPO) — A decoder with enable input can function as demultiplexer that receives information on a single line and terminates on the 2^n o/p lines
 E line of decoder is taken as input line and
 input line of decoder act as select lines
 e.g. If $n=10$ the o/p y_2 will be same as
 E while all other o/p's are maintained at 1
 while all others o/p's are maintained at 1
 * The enable E is also help in cascading decoder

to form larger decoder


e: 4x16 decoder with 3x8 decoder

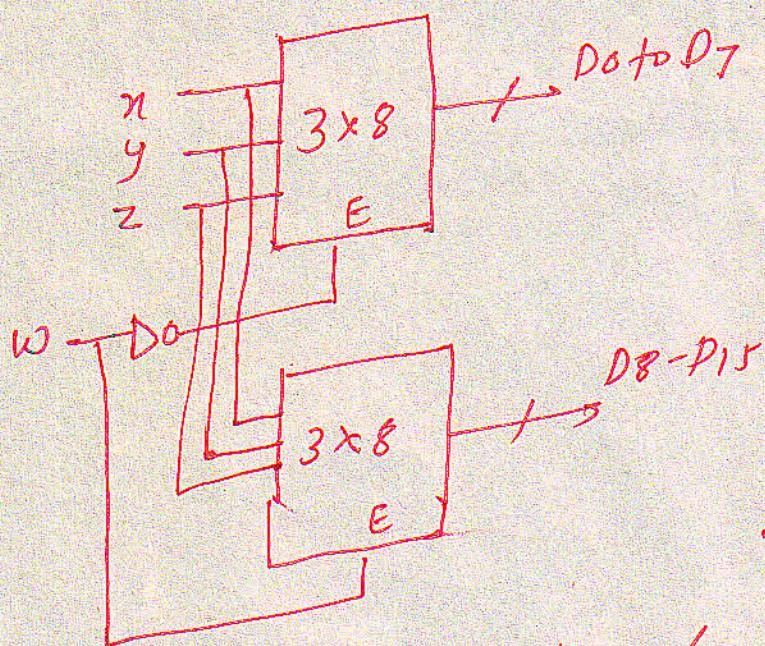


- * If $w=0$ top one's selected and bottom disabled
- * Bottom decoder o/p are held at 0 and top generally the min term. 0000 to 0111

- * If $w=1$ bottom is selected with 1000 to 1111

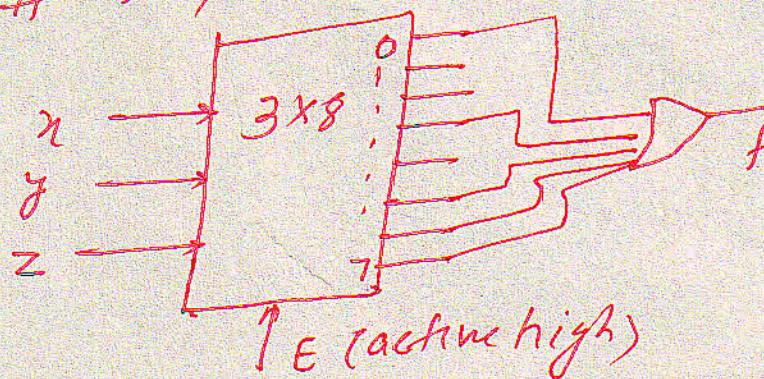Implement with Decoder $f(n, y, z) = \Sigma(0, 3, 5, 6, 7)$


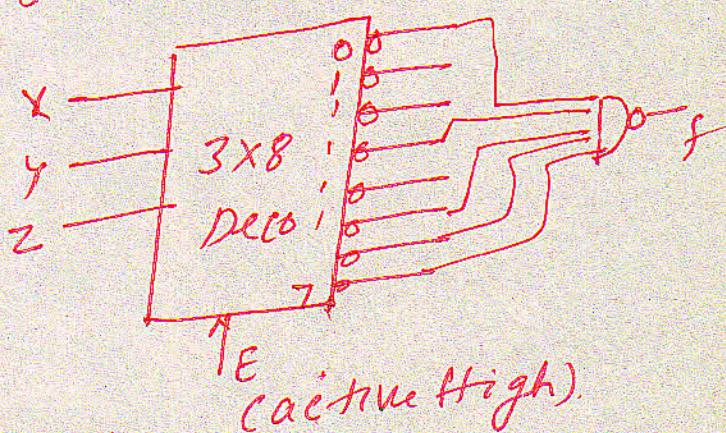
$$\begin{aligned} f &= \text{Decoder + OR active high o/p} \\ &= \text{Decoder + NAND active low o/p} \end{aligned}$$




Implement combinational ckt defined by following function with decoder


$$f_1 = \bar{x}\bar{y} + xy\bar{z} = \Sigma(0, 1, 6)$$

$$f_2 = \bar{x} + y = \Sigma(0, 1, 2, 3, 6, 7)$$

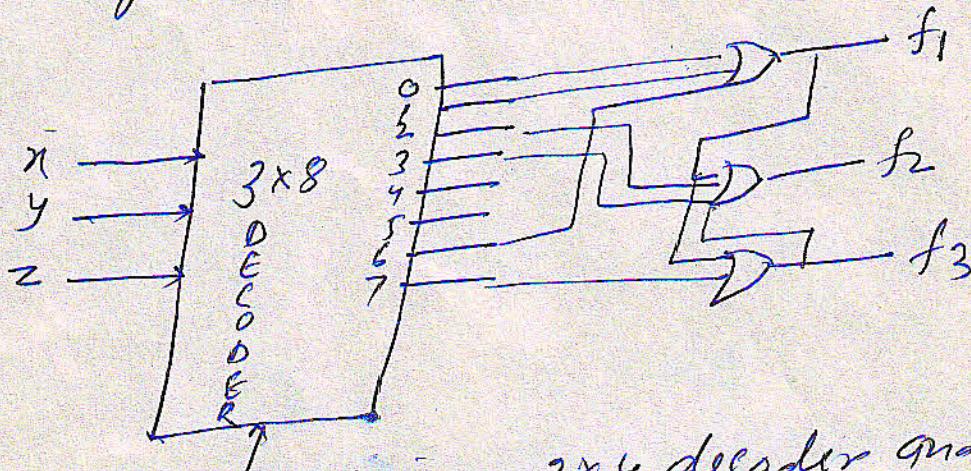
$$f_3 = xy + \bar{x}\bar{y} = \Sigma(0, 1, 6, 7)$$



5x32 decoder using 2x4 decoder and 3x8

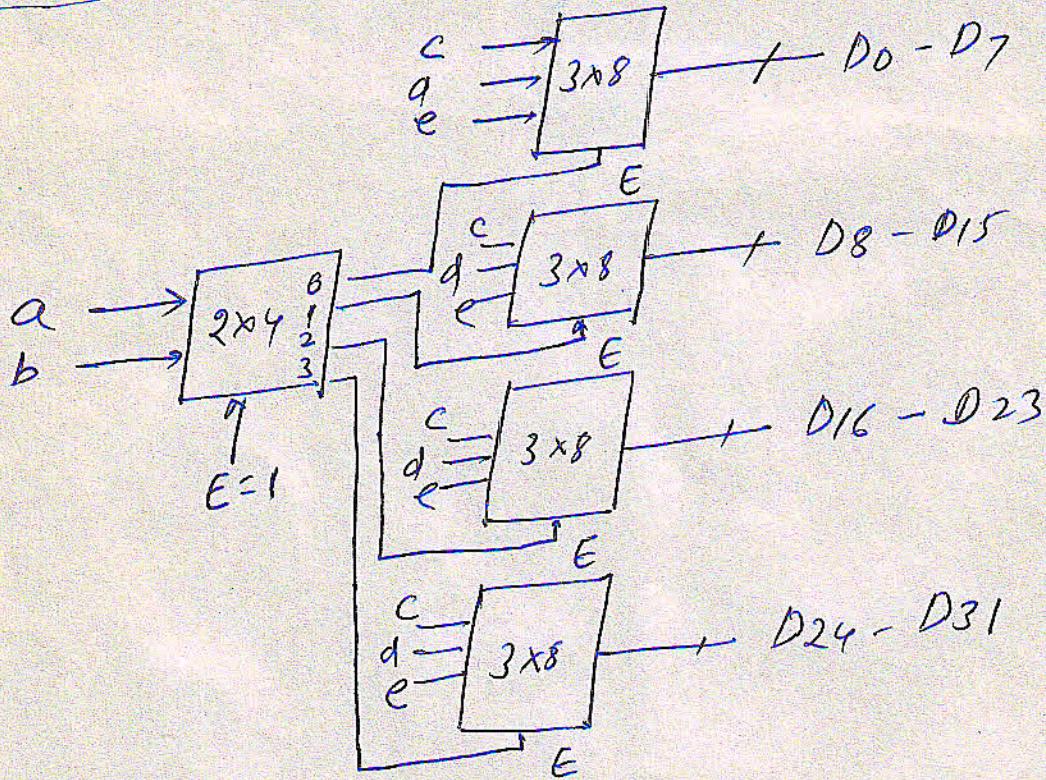

5x32 using 4x16

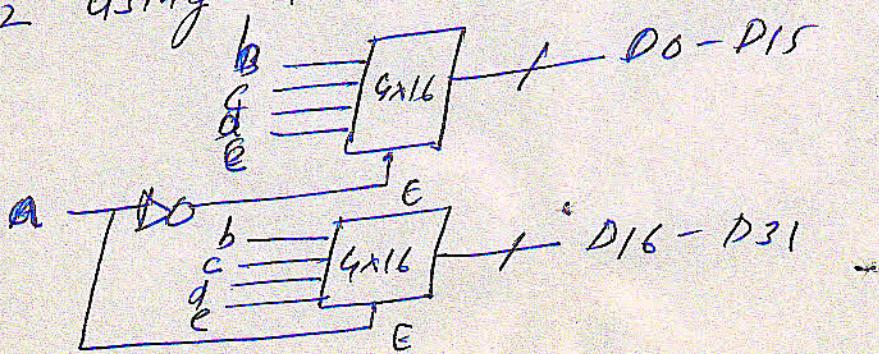


Boolean func with demultiplexer \rightarrow one to many.


Implement FA

$$S = \Sigma(1, 2, 4, 7)$$


$$C = \Sigma(3, 5, 6, 7)$$

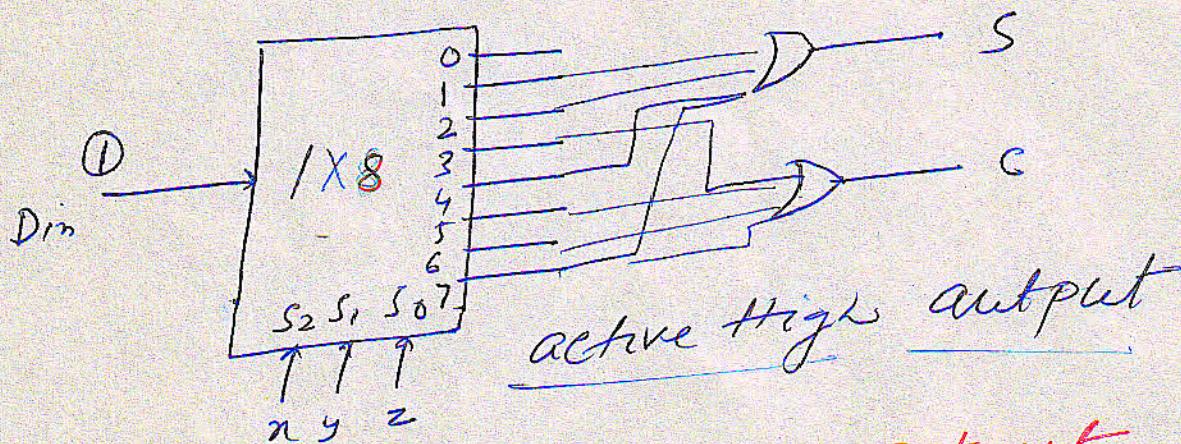

\Rightarrow Demux with active low Output

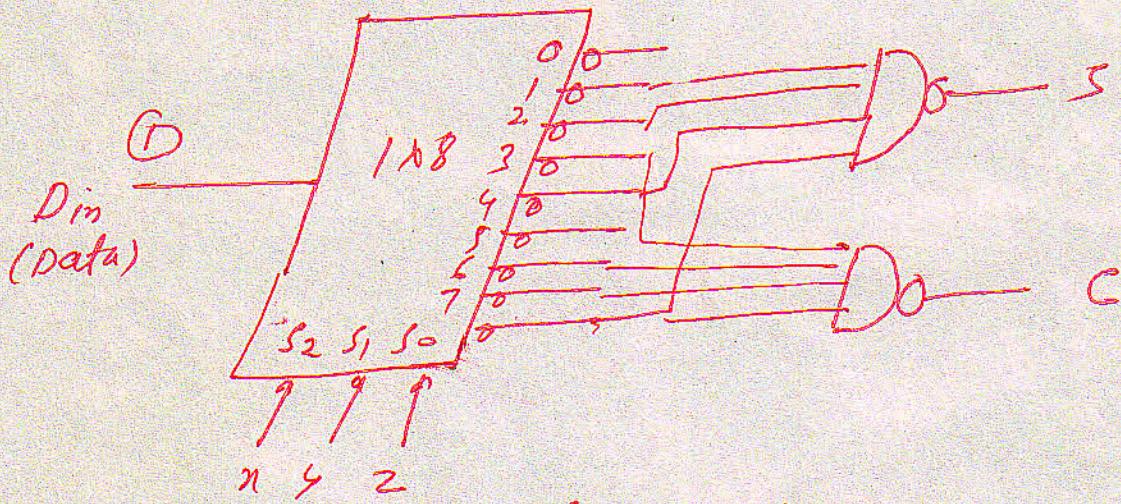

\Rightarrow function table for Demux

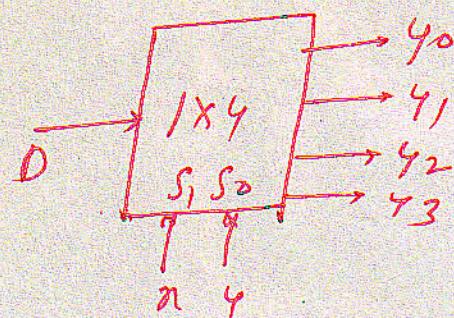


	S_1	S_0	Y_0	Y_1	Y_2	Y_3	$Y_0 = \bar{S}_1 \bar{S}_0 \cdot D$
	0	0	1	0	0	0	$Y_1 = \bar{S}_1 \bar{S}_0 \cdot D$
	0	1	0	1	0	0	$Y_2 = S_1 \bar{S}_0 \cdot D$
	1	0	0	0	1	0	$Y_3 = S_1 \bar{S}_0 \cdot D$
	1	1	0	0	0	1	

\Rightarrow Demux to decoder \rightarrow use Select lines as Input lines and input line as enable line


\Rightarrow Decoder to demux \rightarrow use input lines as select lines and enable input as input line

\Rightarrow 1×4 Demux = 2×4 decoder 1×8 Demux: 3×8 decoder
 $1A16 \quad n \quad n \quad 2 \quad 4A16 \quad n$

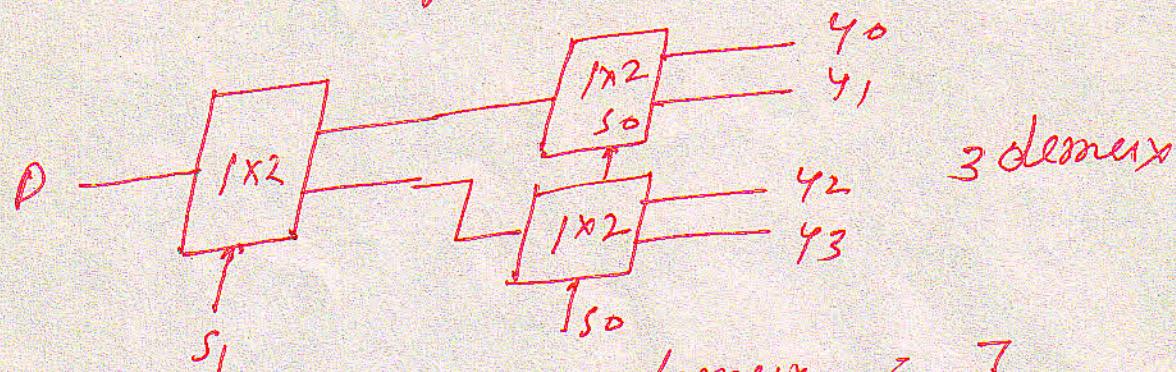\Rightarrow 1:4 demux using 1:2 ^{De} demux




\Rightarrow 1:8 demux using 1:2 demux ^z

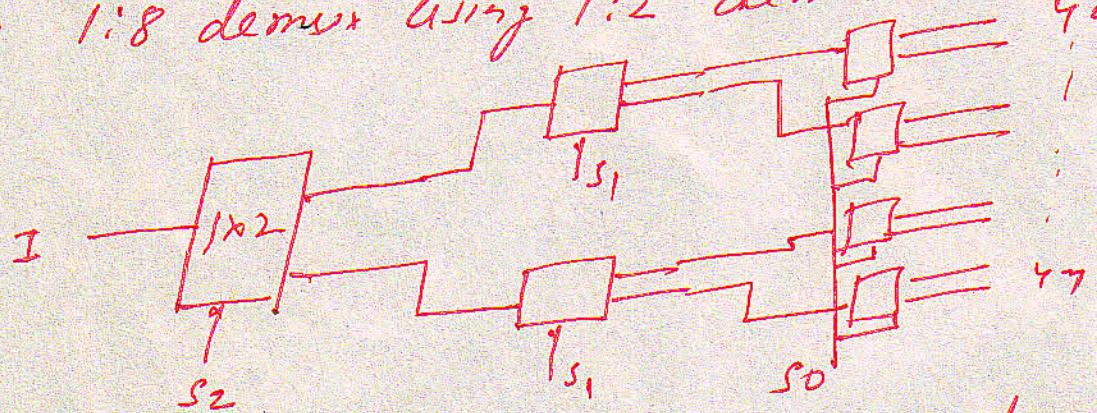

\Rightarrow 1:16 using 1:4 Total 5 demux.

Encoder \rightarrow It does reverse of decoder
It has 2^n (or less) input lines and n O/P lines. The O/P lines generate the binary code for 2^n input combinable i.e. octal to binary encoder

D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

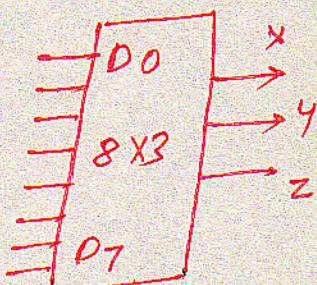


$$x = D_4 + D_5 + D_6 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$z = D_1 + D_3 + D_5 + D_7$$

- * Encoders of this type are not available in IC package. They can be easily constructed with OR logic. The type of encoder available in IC form is called "priority encoder"
- * D_0 is not used in any OR Logic. Binary out put is all 0's in this case. All 0 outputs is also obtained when all inputs are 0's. This discrepancy may be resolved by providing one more output to indicate that all inputs are not 0's.
- * only one input line can be high at any time if two or more input lines are high simultaneously, encoder has no meaning in the sense that it fails to provide an appropriate output.

\Rightarrow 4 line to 2 line encoder

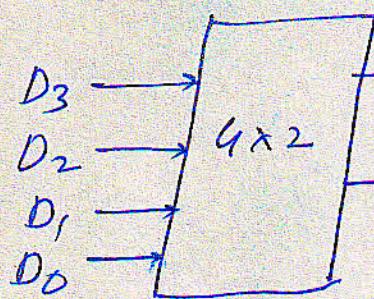

	D_3	D_2	D_1	D_0	Y_1	Y_0
	0	0	0	1	0	0
	0	0	1	0	0	1
	0	1	0	0	1	0
	1	0	0	0	1	1

for remaining
IP comb or
all per one
don't care

$$Y_1 = D_2 + D_3, \quad Y_0 = D_1 + D_3$$

priority encoder \rightarrow In priority encoder inputs are priority $D_3 > D_2 > D_1 > D_0$. don't care not the outputs, for order of

D_3	D_2	D_1	D_0	Y_1	Y_0	$Y_1 = D_2 + D_3$	$Y_0 = D_3 + D_1 \bar{D}_2$
0	0	0	1	0	0		
0	0	1	x	0	1		
0	1	x	x	1	0		
1	x	x	x	1	1		

Code converter — $BCD \rightarrow X-3$

d	b ₃	b ₂	b ₁	b ₀	E ₃	E ₂	E ₁	E ₀	$E_1 = b_1 \oplus b_0, E_0 = \bar{b}_0$
0	0	0	0	0	0	0	1	1	
1	0	0	0	1	0	1	0	0	$E_2 = \bar{b}_2 b_0 + \bar{b}_2 b_1$
2	0	0	1	0	0	1	0	1	+ $b_2 b_1 \bar{b}_0$
3	0	0	1	1	0	1	1	0	
4	0	1	0	0	0	1	1	1	$E_3 = b_3 + b_2 b_0 + b_2 b_1$
5	0	1	0	1	0	1	0	0	
6	0	1	1	0	1	0	0	0	
7	0	1	1	1	1	0	0	1	
8	1	0	0	0	1	0	1	0	
9	1	0	0	1	1	0	1	1	
					1	1	0	0	

Binary \rightarrow Gray.

$$b_3 b_2 b_1 b_0 \rightarrow g_3 g_2 g_1 g_0$$

$$g_3 = b_3$$

$$g_2 = b_3 \oplus b_2$$

$$g_1 = b_2 \oplus b_1$$

$$g_0 = b_1 \oplus b_0$$

Gray to Binary.

$$b_3 = g_3$$

$$b_2 = g_2 \oplus g_3$$

$$b_1 = g_1 \oplus g_2 \oplus g_3$$

$$b_0 = g_0 \oplus g_1 \oplus g_2 \oplus g_3$$

BCD to Gray.

$$g_3 = d_3$$

$$g_2 = d_2 + d_3$$

$$g_1 = d_1 \oplus d_2$$

$$g_0 = d_1 \oplus d_0$$

Gray to BCD

$$d_3 = g_3, d_2 = \bar{g}_3 g_2, d_1 = \bar{g}_2 g_1 + \bar{g}_3 g_2 \bar{g}_1$$

$$d_0 = \bar{g}_1 g_0 + g_1 \bar{g}_0$$


d_3	d_2	d_1	d_0
0	0	0	0
0	0	0	1
0	0	1	1
0	0	1	0
0	0	1	0
0	1	0	1
0	1	0	0
0	1	1	0
0	1	1	1
0	1	0	0
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

$$d_3 = g_3$$

d_2	$\bar{g}_1 \bar{g}_2$	$\bar{g}_1 g_0$	$\bar{g}_1 \bar{g}_0$	$\bar{g}_1 \bar{g}_0$
$\bar{g}_3 \bar{g}_2$	0	0	0	0
$\bar{g}_3 g_2$	1	1	1	1
$g_3 \bar{g}_2$	0	0	x	x
$g_3 g_2$	x	x	x	x

$$= \bar{g}_3 \bar{g}_2$$

And so on.

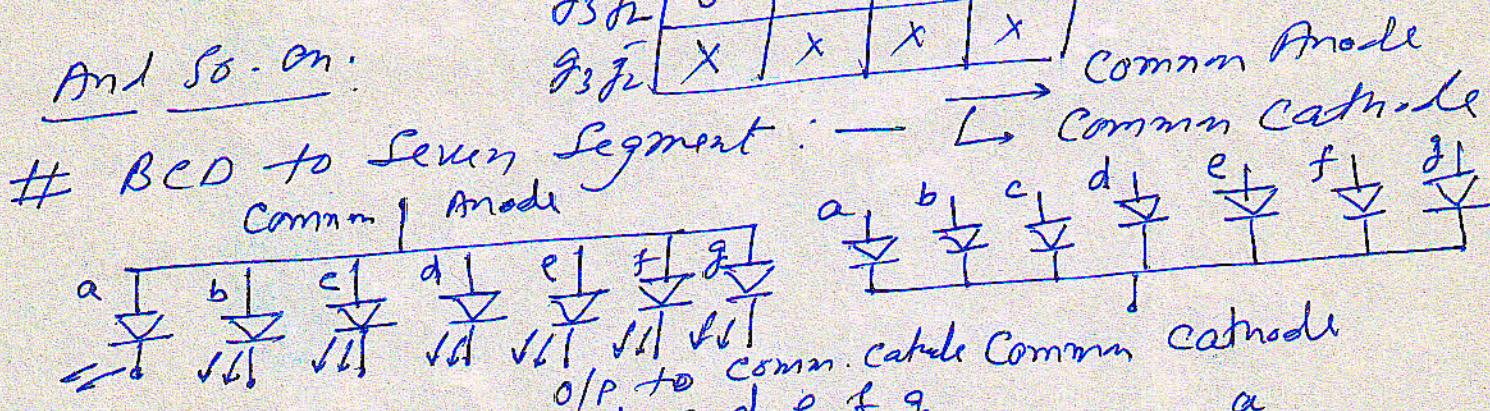

d	b ₃	b ₂	b ₁	b ₀	a	b	c	d	e	f	g
0 → 0	0	0	0	0	1	1	1	1	1	0	0
1 → 0	0	0	0	1	0	0	0	0	0	1	1
2 → 0	0	0	1	0	1	0	0	1	1	1	1
3 → 0	0	0	1	1	0	1	0	0	1	1	1
4 → 0	1	0	0	0	1	1	0	1	1	0	1
5 → 0	1	0	1	0	1	1	1	1	1	0	1
6 → 0	1	1	1	0	1	1	0	0	0	1	1
7 → 0	0	0	0	1	1	1	1	1	1	1	1
8 → 1	0	0	1	1	0	1	1	1	1	1	1
9 → 1	0	0	1	1	1	1	0	1	1	1	1


a, b, c, d, e, f, g
Can be solved
by K-map.

Excm - 3 to BCD Code Converter using Gates (NAND).


Excm - 3

w	n	y	z
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

BCD			
A	B	C	D
x	b	x	x
x	b	b	b
x	x	x	b
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	1	0
1	0	1	1
1	0	0	0
1	0	0	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

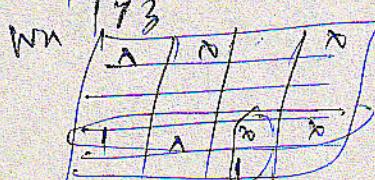


$$A = w_n \cdot w_yz$$

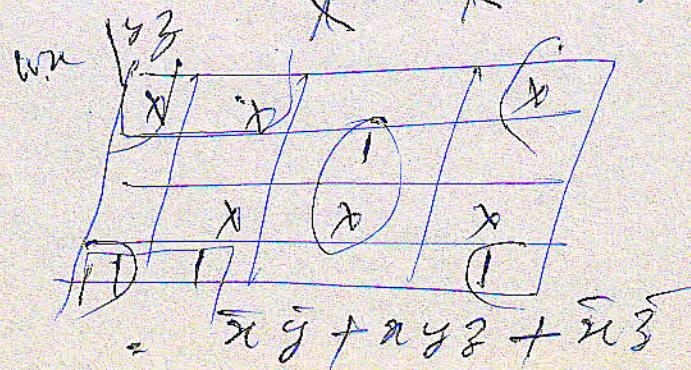


$$= \bar{x}y + x\bar{y}z + \bar{x}z$$

Wn

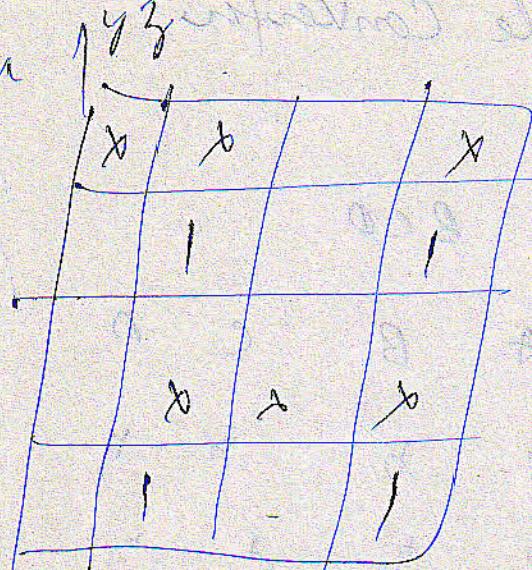

$$c = \bar{y}_3 + y_3$$

Wn

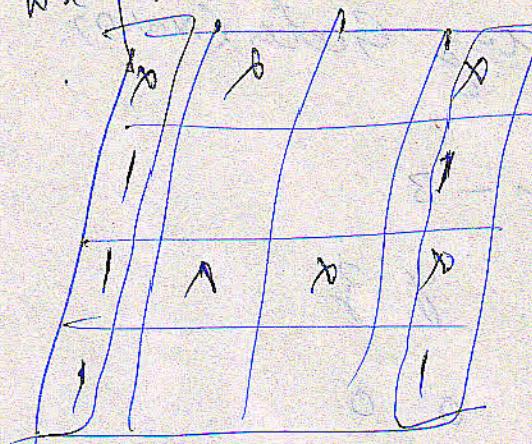

$$D = \bar{z}$$