

Boolean Algebra — George Boole — 1854

It deals with Variable that take on two discrete values 0/1. $A, B, C, x, y, z,$

* Basic logical operation — OR, AND, NOT

OR (Parallel switching ckt)	AND (Series switching ckt)	NOT
$x + 0 = x$	$x \cdot 1 = x$	$x \rightarrow \bar{x}$
$x + 1 = 1$	$x \cdot 0 = 0$	$\bar{x} \rightarrow x$
$x + \bar{x} = 1$	$x \cdot x = x$	$1 \rightarrow 0$
$x + x = x$	$x \cdot \bar{x} = 0$	$0 \rightarrow 1$

→ Dual

$$\begin{array}{ccc} + & \longrightarrow & \cdot \\ \cdot & \longrightarrow & + \end{array}$$

$$x + yz + xy\bar{z} \xrightarrow{\text{Dual}} x \cdot (y+z) \cdot (x+y+\bar{z})$$

⇒ Theorems —

* Commutative —

$$x + y = y + x \xrightarrow{\text{dual}} xy = yx$$

* Associative:

$$x + (y + z) = (x + y) + z \longrightarrow x(yz) = (xy)z$$

* Distributive

$$x(y+z) = xy + xz \longrightarrow x + yz = (x+y)(x+z)$$

* Absorption:

$$x + xy = x \longrightarrow x(xy) \longrightarrow x$$

* De Morgan: $\overline{(x+y+z)} = \bar{x} \cdot \bar{y} \cdot \bar{z} \longrightarrow \overline{xyz}$

* Transposition: $\overbrace{(A+B)(A+C)} = A \cdot A + B \cdot C = A + BC = (\bar{x} + \bar{y} + \bar{z})$

$$\Rightarrow A + \bar{A}B \Rightarrow (A + \bar{A})(A + B) = A + B$$

$$A(\bar{A} + B) = A\bar{A} + AB = AB$$

$$AB + \bar{A}C + BC = (A + BC)(B + BC) + \bar{A}C$$

Redundant
term

$$= (A + B)(A + C)B + \bar{A}C$$

A	BC	$\bar{B}\bar{C}$	$\bar{A}C$	BC	BC
\bar{A}		1	1		
A				1	1

$$\Rightarrow AB + \bar{A}C$$

$$AB + \bar{A}C + B(A + \bar{A})C$$

$$AB + \bar{A}C + ABC + \bar{A}BC$$

$$AB(1 + C) + \bar{A}C(1 + B) = AB + \bar{A}C$$

\Rightarrow Consensus Theorem: - 3 Variable

2-terms.
1 Variable complementarity/uncomp.

$$\rightarrow AC + AB + BC$$

$$A - \text{two terms} = AB + BC$$

$$B - \text{" "}$$

$$C - \text{" "}$$

$$\rightarrow AB + BC + AC = AC + BC$$

$$\rightarrow (A + B)(B + C)(\bar{A} + C) = (\bar{A} + C)(A + B)$$

$$\rightarrow \bar{A}\bar{B} + \bar{A}C + \bar{B}C \Rightarrow \bar{A}C + \bar{B}C$$

$\rightarrow AB + BC + \bar{A}B \rightarrow$ Not containing variable 2 terms.
Hence can not apply Consensus theorem.

$$B(A + \bar{A}) + BC$$

$$B + BC = B(1 + C) = B$$

Boolean function Representation — If there are n variable then 2^n possible combination of these variable. Where as 2^{2^n} distinct Boolean function can be generated.

* Min term (product term) → A product term in which all variable appear either is complemented or uncomplemented form.

* Max term: (sum term) → A sum term in which all the literals appear in complemented or uncomplemented form.

* Boolean function expressed as sum of min terms or product of max terms are said to be in Canonical form.

Canonical form			AND Term. (MIN term) Designation		OR Terms Max Term Term Designation	
x	y	z	Term	Designation	Term	Designation
0	0	0	$\bar{x}\bar{y}\bar{z}$	m_0	$x+y+z$	M_0
0	0	1	$\bar{x}\bar{y}z$	m_1	$x+y+\bar{z}$	M_1
0	1	0	$\bar{x}y\bar{z}$	m_2	.	.
0	1	1	$\bar{x}yz$	m_3	.	.
1	0	0	$x\bar{y}\bar{z}$	m_4	.	.
1	0	1	$x\bar{y}z$	m_5	.	.
1	1	0	$xy\bar{z}$	m_6	.	.
1	1	1	xyz	m_7	$\bar{x}+\bar{y}+\bar{z}$	M_7

$$\Rightarrow (m_5)' = M_5$$

Note: If Boolean function expressed by terms containing one, two or any no. of literals then it is called Standard form.

Standard form

logic 1

SOP

POS

logic 0

* $f(x, y, z) = 1$ has 8 min term. 0 max term

* $f(x, y, z) = 0$ has 0 " " 8 max "

* $f(a, b, c) = a + \bar{b}c$ is in SOP form but not in canonical form.

$$a(b + \bar{b}) = ab + a\bar{b} = ab(c + \bar{c}) + a\bar{b}(c + \bar{c})$$

$$= abc + ab\bar{c} + a\bar{b}c + a\bar{b}\bar{c}$$

$$(a + \bar{a})(\bar{b} + b)c = (a + \bar{a})\bar{b}c = a\bar{b}c + \bar{a}\bar{b}c$$

$$f(a, b, c) = abc + ab\bar{c} + a\bar{b}c + a\bar{b}\bar{c} + \bar{a}\bar{b}c$$

$$= \Sigma(1, 4, 5, 6, 7) = \Sigma = m_1 + m_4 + m_5 + m_6 + m_7$$

* $f(x, y, z) = xy + x'z \leftarrow \text{SOP or } (xy + x')(x'z + z)$

convert in POS

$$f_{\text{dual}} = (x + y)(x' + z) = xx' + xz + x'y + yz$$

$$(f_{\text{dual}})_{\text{dual}} = (x + z)(\bar{x} + y)(y + z)$$

$$= (x + z + yy')(\bar{x} + y + zz') \neq xx' + y + z$$

$$= (x + y + z)(x + y' + z)(\bar{x} + y + z)(\bar{x} + y' + z')$$

$$(x + y + z)(x' + y + z)(x + y' + z)$$

$$= (x + y + z)(x + y' + z)(\bar{x} + y + z)(\bar{x} + y' + \bar{z})$$

$$= M_0 \quad M_2 \quad M_4 \quad M_5$$

$f(x, y, z) = \Pi(0, 2, 4, 5) \rightarrow 4 \text{ Max Terms.}$

$$* f(A, B, C, D) = (AB + CD)(A'B' + C'D')$$

Neither SOP or POS

3.5
 \Rightarrow * If there are two Boolean functions F_1 and F_2
 then $G = F_1 + F_2 \rightarrow$ contain all the min terms of F_1 and F_2
 $E = F_1 \cdot F_2 \rightarrow$ only common min terms of F_1 and F_2

\Rightarrow dual \rightarrow Dual are used to convert +ve logic to neg logic

$+ \rightarrow 0$
 $0 \rightarrow +$
 $1 \leftrightarrow 0$

Keep literal as it

Self dual \rightarrow If the dual of a function is function itself then it is called Self dual
 with n variable Max possible self dual function are $2^{2^{n-1}}$

Complements \rightarrow



- (i) AND \leftrightarrow OR \rightarrow dual
- (ii) $1 \leftrightarrow 0$
- (iii) Complements each literals

$$f = \bar{x} \cdot y \cdot \bar{z} + \bar{x} \bar{y} z$$



$$f_{\text{dual}} = (\bar{x} + y + \bar{z}) (\bar{x} + \bar{y} + z)$$

$$f' = (x + \bar{y} + z) (x + y + \bar{z})$$

Venn diagram: —

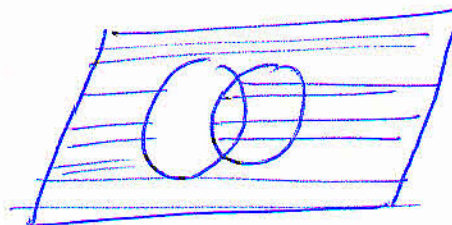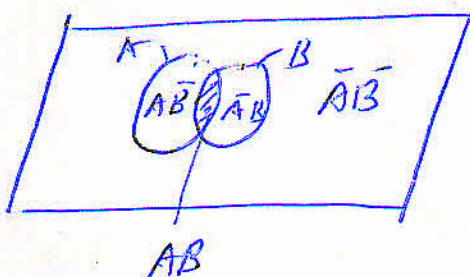
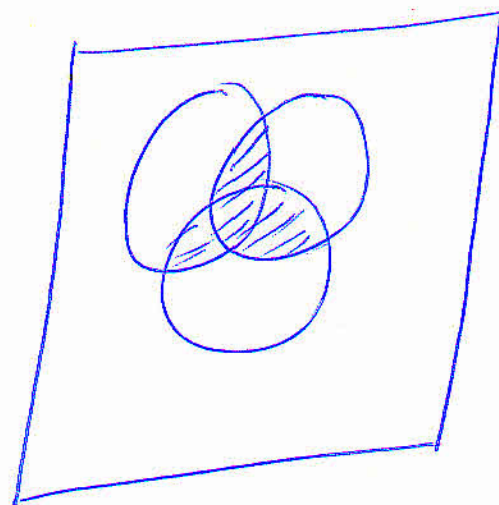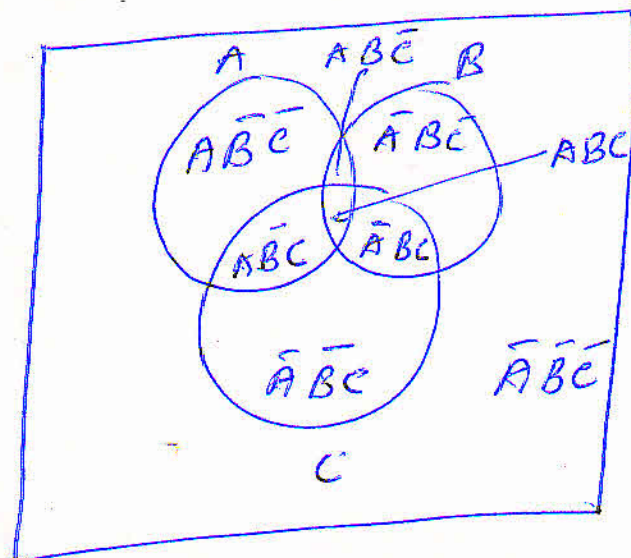
$$AB + \bar{A}\bar{B} + \bar{A}B = \bar{A} + B$$



$$\begin{aligned}
 & ABC + \bar{A}BC + A\bar{B}C \\
 & + A\bar{B}\bar{C} \\
 & = AB + BC + AC
 \end{aligned}$$

⇒ TRUTH TABLE ⇒



x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

in
SOP $F = m_1 + m_4 + m_7$
 $= \bar{x}\bar{y}z + x\bar{y}z + xyz$
 $F = \Sigma[1, 4, 7]$


in
SOP POS
 $F = M_0 M_2 M_3 M_5 M_6$
 $= \Pi(0, 2, 3, 5, 6)$

$$\begin{aligned}
 F &= (x + y + z)(x + \bar{y} + z) \\
 &\quad (x + \bar{y} + \bar{z})(\bar{x} + y + \bar{z}) \\
 &\quad (\bar{x} + \bar{y} + z)
 \end{aligned}$$


⇒ Switching Circuit Representation →

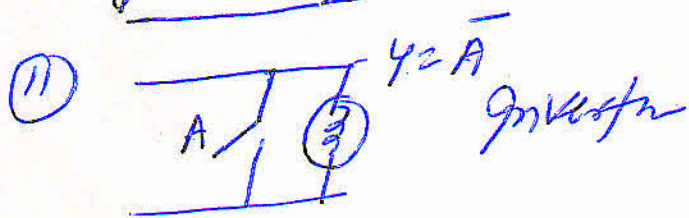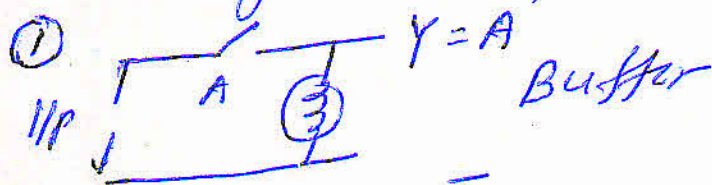


A	y	open → logic 0
0	0	close → logic 1
1	1	
A	y	or vice versa
0	1	
1	0	

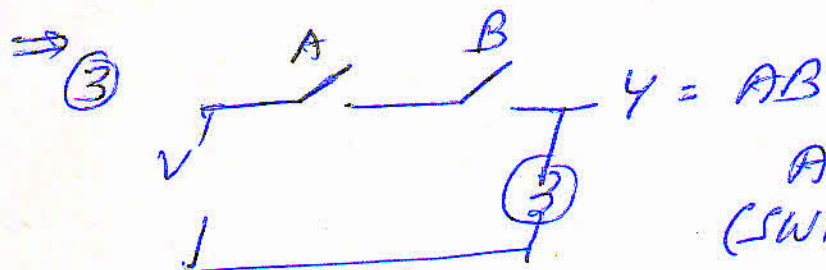


AND Gate.
(Switch are in series).

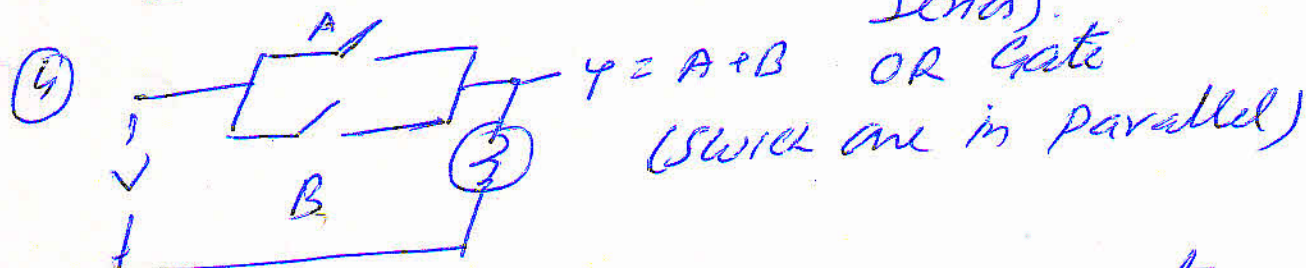



OR Gate
(Switch are in parallel)

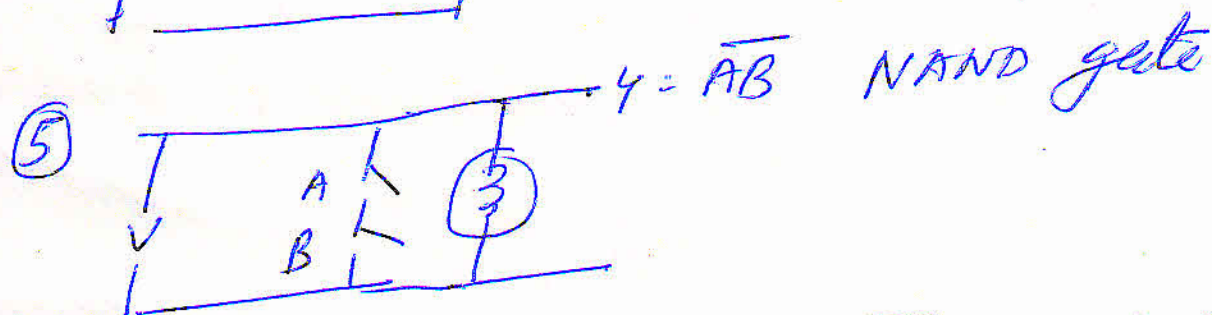


NAND gate

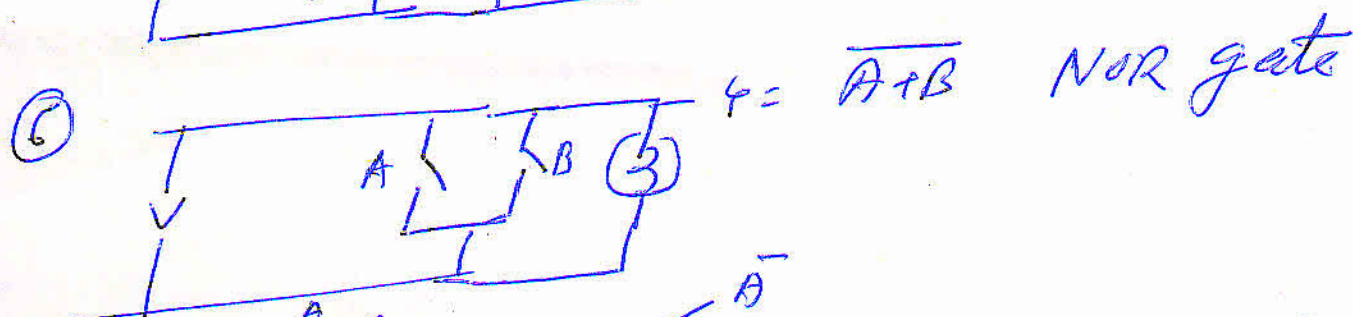

NOR gate

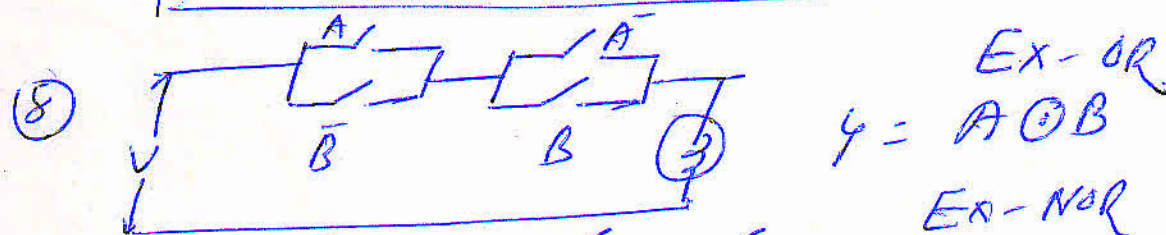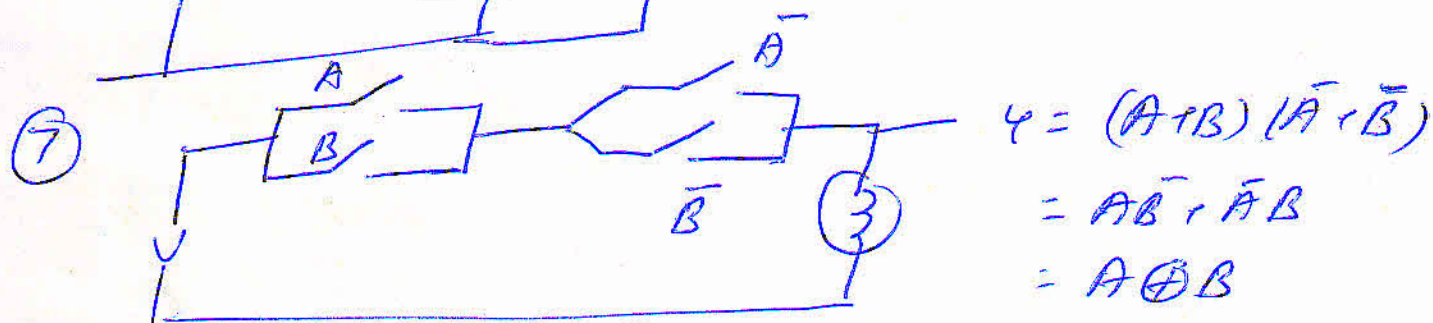


EX-NOR

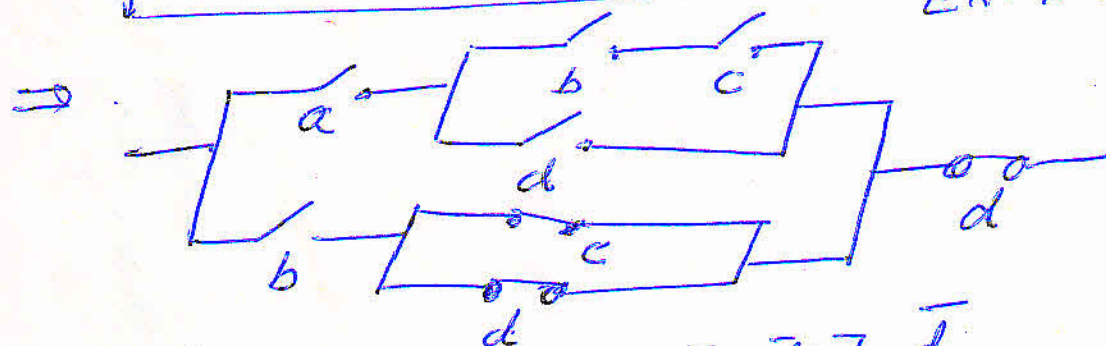

$$[a \cdot (bc + d) + b \cdot (c\overline{c} + d)] \cdot \overline{d}$$
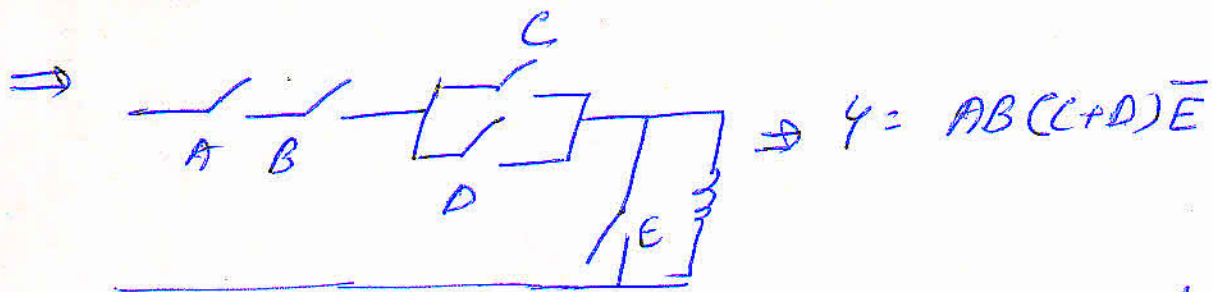
$$= abc\overline{d} + b\overline{c}\overline{d} + b\overline{d}$$



⇒ A logic ckt Have three Input A, B, C. and O/P Y
Have logic 1 from the following condition.

- I) A & B are false
- II) A & C " True
- III) A, B & C " false
- IV) A, B & C " True

$$\begin{aligned}
 Y &= \bar{A}\bar{B} + AC + \bar{A}B\bar{C} + ABC \\
 &= \bar{A}\bar{B}(1+C) + AC(1+B) \\
 &= \bar{A}\bar{B} + AC
 \end{aligned}$$

⇒ Example ⇒

$$A \quad AB + ABC + A\bar{B} = A$$

$$AB(1+C) + A\bar{B} = AB + A\bar{B} = A(B + \bar{B}) = A$$

$$* \quad (a+b)(b+d)(a+c)(c+d) = bc + ad$$

$$(b+ad)(c+ad) = bc + ad$$

$$\frac{x}{x} \quad \frac{z}{z} \quad \frac{y}{y} \quad \frac{z}{z} \quad (xy + z)$$

$$* \quad (\bar{A} + B)\bar{A}\bar{B}\bar{C} = \overline{A+B+C} = \bar{A}\bar{B}\bar{C}$$

$$\bar{A}\bar{A}\bar{B}\bar{C} + \bar{A}B\bar{B}\bar{C} = \bar{A}\bar{B}\bar{C} = \overline{A+B+C}$$

$$* \quad a + b + \bar{c}\bar{d} = \bar{a}b + \bar{a}\bar{c} + \bar{a}\bar{d}$$

$$\begin{aligned}
 \overline{a + b + (\bar{c} + \bar{d})} &= \overline{a + b + cd} = \bar{a} \cdot (b + \bar{c} + \bar{d}) \\
 &= \bar{a}b + \bar{a}\bar{c} + \bar{a}\bar{d}
 \end{aligned}$$